

DESIGNCON 2012

WHERE CHIPHEADS CONNECT



TecForum TF-MP2: Dynamic Characterization of DC-DC Converters




DESIGNCON 2012

WHERE CHIPHEADS CONNECT



Disclaimer:

This presentation does not constitute as an endorsement for any specific product, service, company, or solution.

 

DESIGNCON 2012

WHERE CHIPHEADS CONNECT



Part I: Dynamic Characterization of DC-DC Converters from a System's Perspective

Istvan Novak, Oracle-America Inc.

Kendrick Barry Williams, Oracle-America Inc.

Chris Young, Intersil Corporation

Brandon Howell, Intersil Corporation

Jason R. Miller, Oracle-America Inc.

Gustavo Blando, Oracle-America Inc.

DESIGNCON 2012

WHERE CHIPHEADS CONNECT



Part II: Power Filter Network and its Effect on DC-DC Converters

Kendrick Barry Williams, Oracle-America Inc.

Istvan Novak, Oracle-America Inc.

Brandon Howell, Intersil Corporation

Chris Young, Intersil Corporation



Outline

Part I: Dynamic Characterization of DC-DC Converters from a System's Perspective

- **I. Introduction and background**
 - Dynamic specification items
 - Output filter
 - Modulator
 - Error amplifier and Loop compensation
- **II. Dynamic parameters of DC-DC converters from a system's perspective**



Outline (continued):

- **III. Output impedance of DC-DC converters**
 - How source impedance influences output impedance
 - Multiple Converters in Parallel
 - Observations and Assumptions
 - Digital Control
- **IV. Measurements, Modeling, Simulations**
 - Measurements
 - Modeling, simulations
- **Conclusions**



Outline

Part II: Power Filter Network and its Effect on DC-DC Converters

- **I. Introduction and Background Information**
 - DC Converters Introduction
 - Power Filter Introduction
 - DC Converter Specifications
 - Filter Specifications
 - The DC Converter Application
 - Cross-Over Frequency



Outline (continued)

- Power Filter Application
 - Filter input impedance, converter looking toward the load
 - Filter input impedance, the load looking toward the converter
 - Filter Inductor
- **II. Actual Circuit Used and Measurements**
 - Added Bulk Capacitors Removed
- **Summary**




Motivation

- Number of DC-DC converters is on the rise
- Dynamic noise allowance keeps shrinking
- Recent converter trends offer new solutions



Quiz Question 1

 
- Which step response will guarantee smaller worst-case noise A or B?





Quiz Question 2

 - Which impedance profile will guarantee smaller worst-case noise, A or B?





Quiz Question 3

- In what frequency range will the converter loop influence transient response and output impedance?
 - Up to 10x the cross-over frequency
 - Not above the cross-over frequency
 - Up to 2x the cross-over frequency





Outline

Part I: Dynamic Characterization of DC-DC Converters from a System's Perspective

- **I. Introduction and background**
 - Dynamic specification items
 - Output filter
 - Modulator
 - Error amplifier and Loop compensation
- II. Dynamic parameters of DC-DC converters from a system's perspective




Non-isolated Buck Converter

  

$$V_{out} = D V_{in}$$



The Feedback Loop

 

$$G_{loop} = G_M G_F G_C G_{EA}$$




Dynamic Parameters

- Loop stability is the most important
- Load response or output impedance
- Line response, input impedance
- Output ripple, ringing noise



Output Filter in Voltage-Mode Control

 

$$G_F = \frac{Z_{Load} \parallel Z_C}{Z_L + Z_{Load} \parallel Z_C}$$




G_F Transfer Function

Assume infinite load impedance

$$G_F = \frac{1 + j\omega ESR C}{1 + j\omega(R_{dc} + ESR)C - \omega^2 LC} = \frac{1 + j\omega ESR C}{1 + jQ^{-1} \frac{\omega}{\omega_0} - \left(\frac{\omega}{\omega_0}\right)^2}$$

 
$$Q = \frac{\sqrt{L/C}}{R_{dc} + ESR} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$






G_F Transfer Function

Normalized view:

 


A typical plot:

 

Assume infinite load impedance



Modulator

 

$$G_M = \frac{V_{in}}{V_{osc}}$$





Error Amplifier and Loop Compensation

- PID (**P**roportional-**I**ntegral-**D**erivative)
- Type I (Integral)
- Type II (Integral-Proportional)
- Type III (Integral-Proportional-Derivative)





Type I Compensation

 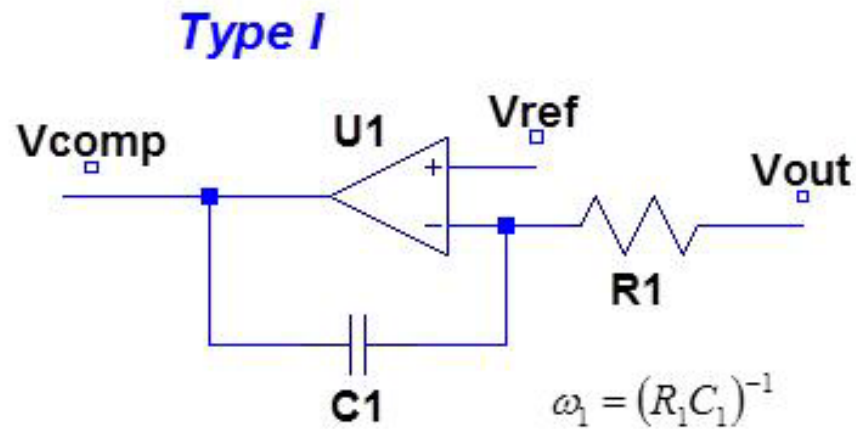




Type II Compensation

  



Type III Compensation

Type III

 

$$\omega_{12} = (R_2(C_1 \parallel C_2))^{-1}$$


$$\omega_{13} = (C_3(R_1 + R_3))^{-1}$$

$$\omega_1 = (R_1 C_1)^{-1}$$

$$\omega_2 = (R_2 C_2)^{-1}$$



$$\omega_3 = (R_3 C_3)^{-1}$$
 
$$G_C G_{EA} = j \frac{\omega_1}{\omega} \frac{\omega_2 + j\omega}{\omega_{12} + j\omega} \frac{R_1 + R_3}{R_3} \frac{\omega_{13} + j\omega}{\omega_3 + j\omega}$$






A Type III Implementation

  



Putting the Loop Together

 



A typical loop gain plot for voltage-mode control with Type III compensation.

Important parameters:

- Cross-over frequency
- Phase margin
- Gain margin




Closed-Loop Output Impedance

  

$$Z_{out-closed-loop}(f) = \frac{Z_{out-open-loop}(f)}{1 + G_{loop}(f)}$$



Line Regulation

 

$$\frac{V_{out}}{V_{in}} = \frac{G_M G_F}{1 + G_{loop}}$$




Outline

Part I: Dynamic Characterization of DC-DC Converters from a System's Perspective

- I. Introduction and background
 - Dynamic specification items
 - Output filter
 - Modulator
 - Error amplifier and Loop compensation
- **II. Dynamic parameters of DC-DC converters from a system's perspective**



The Reverse Pulse Technique

 


Assumptions:

- PDN is LTI
- Random current steps
- Bounded step size
- Bounded step speed




The Reverse Pulse Technique

 Worst-case peak-to-peak transient:
 $V_{pp} = 2 \cdot V_p - V_{DC}$




Worst-case positive response [V]

 




Noise vs. Impedance Profile

 




Noise vs. Impedance Profile

 




Impedance Matching in PDN

 Impedance magnitude of two non-matched parallel capacitors [ohm]



 Impedance magnitude of two matched parallel capacitors [ohm]







Outline (continued):

- **III. Output impedance of DC-DC converters**
 - How source impedance influences output impedance
 - Multiple Converters in Parallel
 - Observations and Assumptions
 - Digital Control
- **IV. Measurements, Modeling, Simulations**
 - Measurements
 - Modeling, simulations
- **Conclusions**





Open-Loop Output Impedance

  





Closed-Loop Output Impedance

  



  Closed-Loop Output Impedance vs. Crossover Frequency






Outline (continued):

 - **III. Output impedance of DC-DC converters**
 - How source impedance influences output impedance
 - Multiple Converters in Parallel
 - Observations and Assumptions
 - Digital Control
- **IV. Measurements, Modeling, Simulations**
 - Measurements
 - Modeling, simulations
- **Conclusions**




Output Impedance, $V_{in} = 3.3V$

Impedance magnitude at $V_{in} = 3.3V$ [ohm]



Impedance Magnitude, Phase [ohm, deg]

 


$V_{out} = 1.8V$, 4A max rated current




Output Impedance, $V_{in} = 5.0V$

 Impedance magnitude at $V_{in} = 5.0V$ [ohm]





Impedance Magnitude, Phase [ohm, deg]

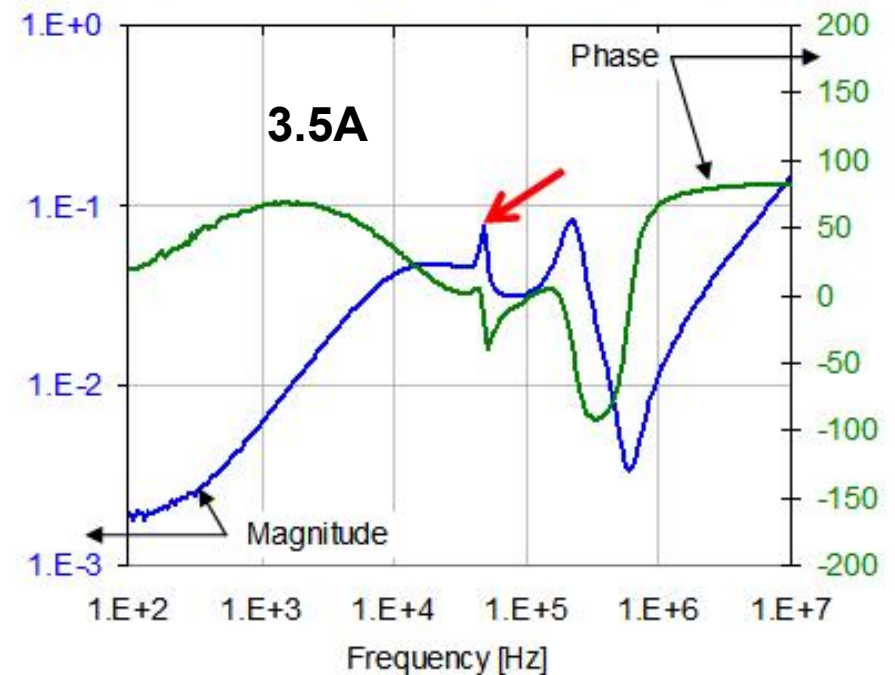

$V_{out} = 1.8V$, 4A max rated current



Output Impedance vs. Gain-Phase

  


$V_{in} = 3.3V$, $V_{out} = 1.8V$, 2A max rated current




Output Impedance vs. Time Domain

 Impedance magnitude at $V_{in} = 3.3V$ [ohm]




Impedance Magnitude, Phase [ohm, deg]

 

$V_{in} = 3.3V$, $V_{out} = 1.8V$, 6A max rated current





Output Impedance vs. Time Domain

 

$V_{in} = 3.3V$, $V_{out} = 1.8V$, 6A max rated current



Impedance Across Input

 
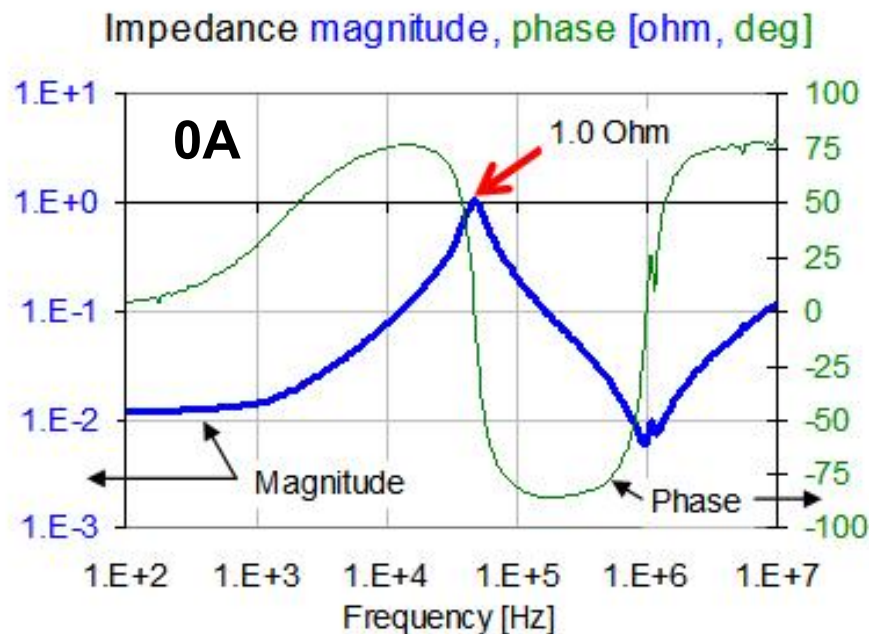


$V_{in} = 3.3V$, $V_{out} = 1.8V$, 4A max rated current

Peak increases with load current




Input vs. Output Impedance

  



Impedance Model of Source/Input

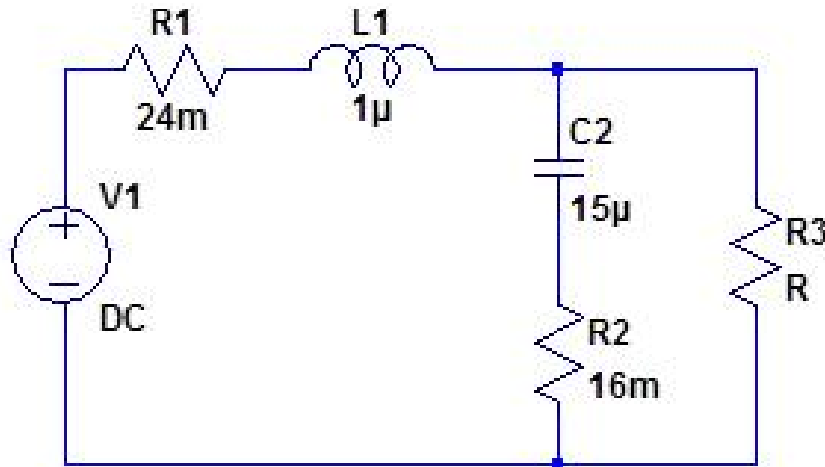

Critical negative load resistance:


$$R_3 = -\frac{R_1 R_2 C + L}{C(R_1 + R_2)}$$

$$r_{in} = \frac{\Delta V}{\Delta I_{in}} = \frac{\Delta V}{\frac{V_{out} I_{load}}{\eta(V_{in} + \Delta V)} - \frac{V_{out} I_{load}}{\eta V_{in}}} = -\eta \frac{V_{in}^2}{V_{out} I_{load}} = -R_{DC}$$




Input Peaking: The Solution

 Impedance magnitude at $V_{in} = 3.5V$ [ohm]



Impedance Magnitude, Phase [ohm, deg]

 

330 μF 25 mOhm polymer capacitor across input

DESIGNCON 2012

WHERE CHIPHEADS CONNECT




Multiple Converters in Parallel



Multiple Converters in Parallel

 - In Multi-phase systems, each phase must share current.
- Current share eases design requirements on each phase
- Current share is both a static and dynamic requirement.





Multiple Converters in Parallel

- In a multi-phase system, each phase can be represented by its Thevenin equivalent
- This allows the system to be simplified into the parallel combination of source impedances, Z_i .

$$\frac{1}{Z_S} = \frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_N} = \frac{N}{Z_i}$$



Multiple Converters in Parallel

- The power system and load share a common voltage (across the load). At medium frequencies the impedance of the passive output network scales with the number of phases.

Or

$$Z_s = \frac{Z_i}{N}$$
$$N \cdot Z_s = Z_i$$



Multiple Converters in Parallel

- So what does this mean?


$$N \cdot Z_S = Z_i$$

- ... the dynamics of a multiphase system can be scaled to the dynamics of a single phase system with load impedance, Z_L , scaled by the number of phases!




Supplies OFF Output Impedance

Impedance magnitude, OFF [ohm]

 

Impedance magnitude ratios, OFF [-]

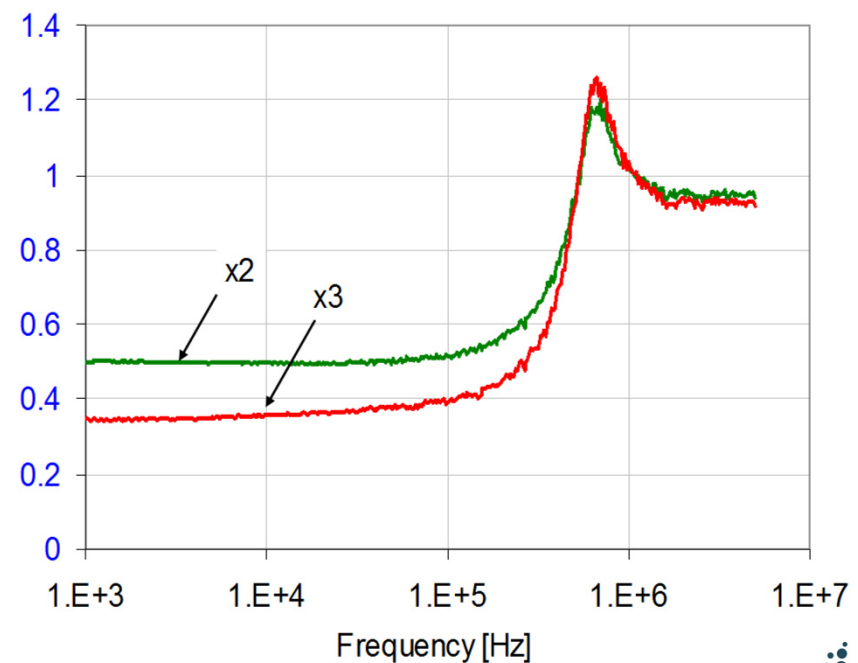




Supplies OFF – Main Points

- For low frequencies, OFF impedance scales with number of supplies added
- As frequency increases, series parasitic inductance between supplies isolates supplies, so parallel supplies have diminishing effect.
- What happens when the supplies are turned on?




Supplies ON, 5A Load

Impedance magnitude, ON, 5A [ohm]

 


Impedance magnitude ratios, ON, 5A [-]

 




Supplies ON, 15A Load

Impedance magnitude, ON, 15A [ohm]

 

Impedance magnitude ratios, ON, 15A [-]

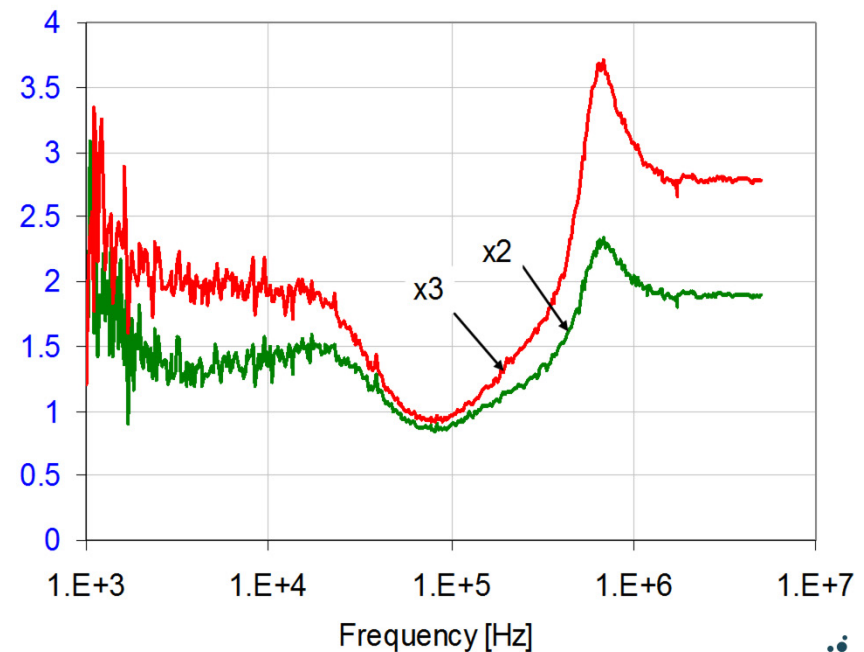



Supplies ON – Main Points

- At low frequencies the high DC loop gain establishes very low impedance, which gets masked out by residual connection resistance - no difference in single, two or three phase plots.
- As frequency increases, loop gain decreases, and impedance distributes according to passive impedance of each phase.
- At high frequencies, parastics dominate.






Multiple Converters in Parallel

- What about the time domain?
- Switching of paralleled converters are typically phase shifted by $360^\circ/N$, where N is the number of supplies
- Do we see similar scaling in output voltage ripple?

DESIGNCON 2012

WHERE CHIPHEADS CONNECT

   



Vout Ripple Scaling



- Dominate contribution of Vout ripple is inductor ripple current multiplied across output capacitor ESR.

$$V_{\text{out_ripple}} = I_{L_{\text{Pk-pk}}} \bullet \text{ESR}_{C_{\text{out}}}$$

- By phase shifting the switching by $360^\circ/N$, effective switching frequency increases, resulting in a decrease in Vout ripple.
- What if phase shifting is disabled?

DESIGNCON 2012

WHERE CHIPHEADS CONNECT

  



Why multiphase?

- When properly designed, current is divided between phases – makes design of 30A+ buck converters realizable and cost effective.
 - Distributes the thermal loading
 - Small, cost effective inductors
- Output impedance scales with number of phases added.
- When phases are phase shifted, Vout ripple scales with number of phases.

DESIGNCON 2012

WHERE CHIPHEADS CONNECT



Digital Control



UBM
Electronics



Digital Control


- Digital Control is rising in popularity
- Many different techniques, but same basic result – produce PWM pulse using digital techniques.
- Analog control uses analog filters in control loop; Digital control uses digital filters, which combine current and historical gained values.




Advantages to Digital Power

- **Programmability/Configurability**
 - Software and Hardware
 - More sophisticated algorithms
 - Control
 - Monitoring
- **Components**
 - Storage
 - Math operations
- **Numerical Stability (e.g. drift)**
 - Calibration
- **Silicon Processes**
- **Resistance to noise**

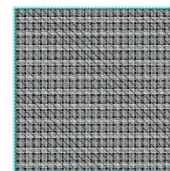
Reduced component count
Higher Density
Lower (system) cost
Better reuse
Faster time to market




100 pf

 


MCU

 

A/D

 


Pad

 


• Analog

 - Well understood
- External control and compensation components



• “Textbook” Digital

- DSP – brute force=\$

 


• Power Optimized Digital

- Efficient compensation
- Strap configurable



Digital PID Filter

 

$$G_d = \frac{A + Be^{-sT} + Ce^{-2sT}}{e^{-sT}(1 - e^{-sT})}$$





Digital PID Filter

$$G_d = \frac{A + Be^{-sT} + Ce^{-2sT}}{e^{-sT}(1 - e^{-sT})}$$

- A, B and C are gain coefficients for various “taps”.
- First term in denominator is due to delays in signal path
- T is the switching frequency of the PWM



Digital PID Filter

- Digital PID compensator has two Zeros, a pole at zero and a pole at infinity.
- Two zeros can be either real or a complex conjugate pair.
- Not limited to just real zeros like in a Type III analog compensator!




Other Advantages...

- **Compensation values are stored in digital registers – no need for solder iron to change compensation!**
- **Automatic compensation algorithms – controller can automatically characterize and compensate plant.**
- **Non-linear control algorithms can easily be implemented.**




What is Non-linear Control?

 - Fast control loop which by-passes normal, slower, PID control loop.
- Many ways to implement – one example is a threshold based approach.
- Net effect is to increase effective control loop bandwidth.





 - Neat, but does it show up in output impedance measurements?







- **No, not in small signal output impedance measurements.**
- **Excitation signal is not large enough to excite NLR response.**
- **What about time domain?**

DESIGNCON 2012

WHERE CHIPHEADS CONNECT

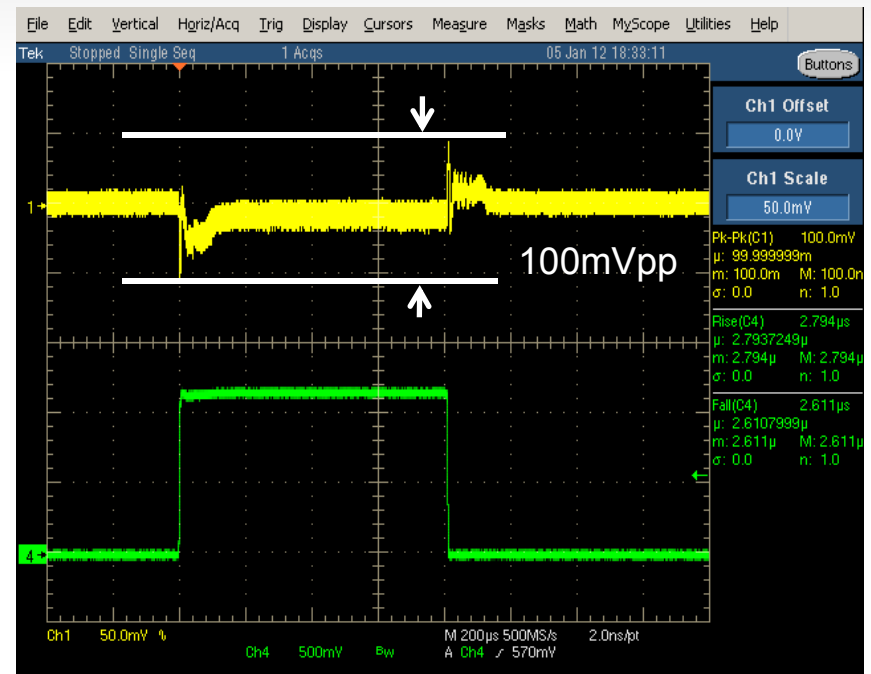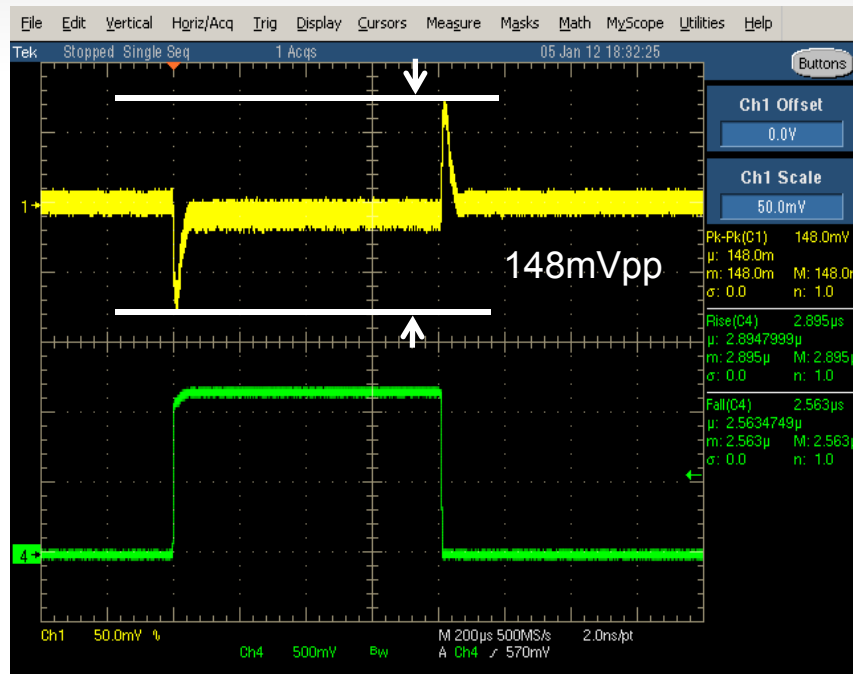

- 33% Reduction in output deviation with NLR!




Outline (continued):

- **III. Output impedance of DC-DC converters**
 - How source impedance influences output impedance
 - Multiple Converters in Parallel
 - Observations and Assumptions
 - Digital Control
- **IV. Measurements, Modeling, Simulations**
 - Measurements
 - Modeling, simulations
- **Conclusions**





Gain-Phase Measurement

 




Gain-Phase Results (1)

  




Gain-Phase Results (2)

 


Instrument
noise floor

 

Error amplifier
saturation




Measuring Low Impedances The Problems

 

- Problems with one-port impedance measurements:
- Discontinuity is in series to the unknown low impedance
 - Reflection reading is not accurate for large reflections



Measuring Low Impedances The Solution

 

Benefits of two-port impedance measurements:


- Discontinuity is in series to the 50-Ohm VNA impedance
- Small DUT voltage is measured by a separate input (Kelvin connection)



Measuring Full Systems (1)




Ferrite isolation with
grounded ports

 


DC power splitter with
floating-ground inputs



Measuring Full Systems (2)

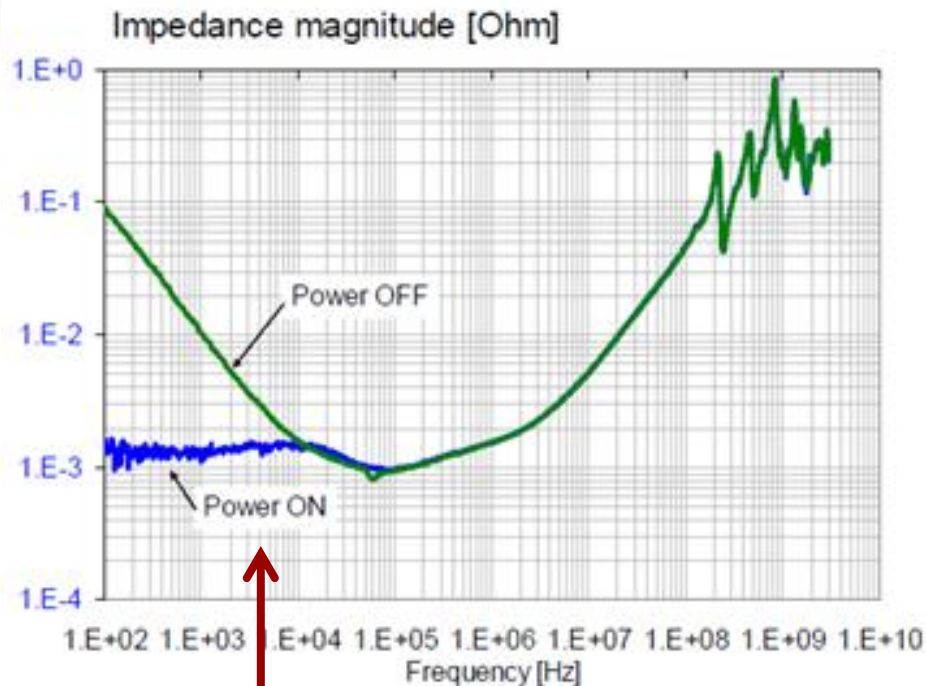


Correct reading with
ferrite isolation

 

Incorrect reading
without ferrite isolation




Large-Signal Z_{out} Measurement

 





Load Transient Measurement

 



Multi-Purpose Test Setup

 


 

Large-Signal Output Impedance Measurement Setup




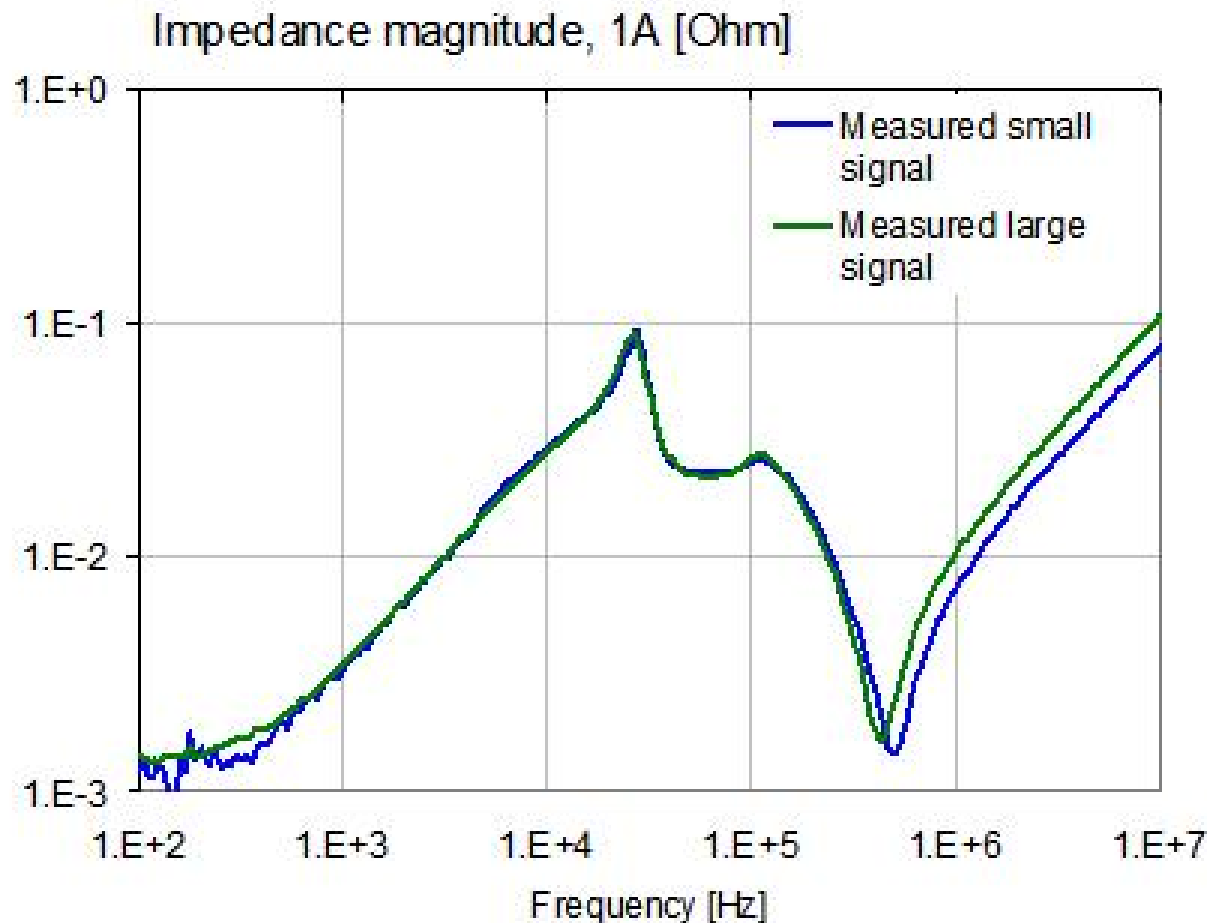Small-Signal vs. Large-Signal Output Impedance






Output Impedance from Step Response

 

- The noise transfer function is V_{out}/i_{load}
- The Fourier Transform of the transfer function is the Impulse Response
- The Step Response is the integral of the Impulse Response




Step Response

 



Z_{out} from Step Response

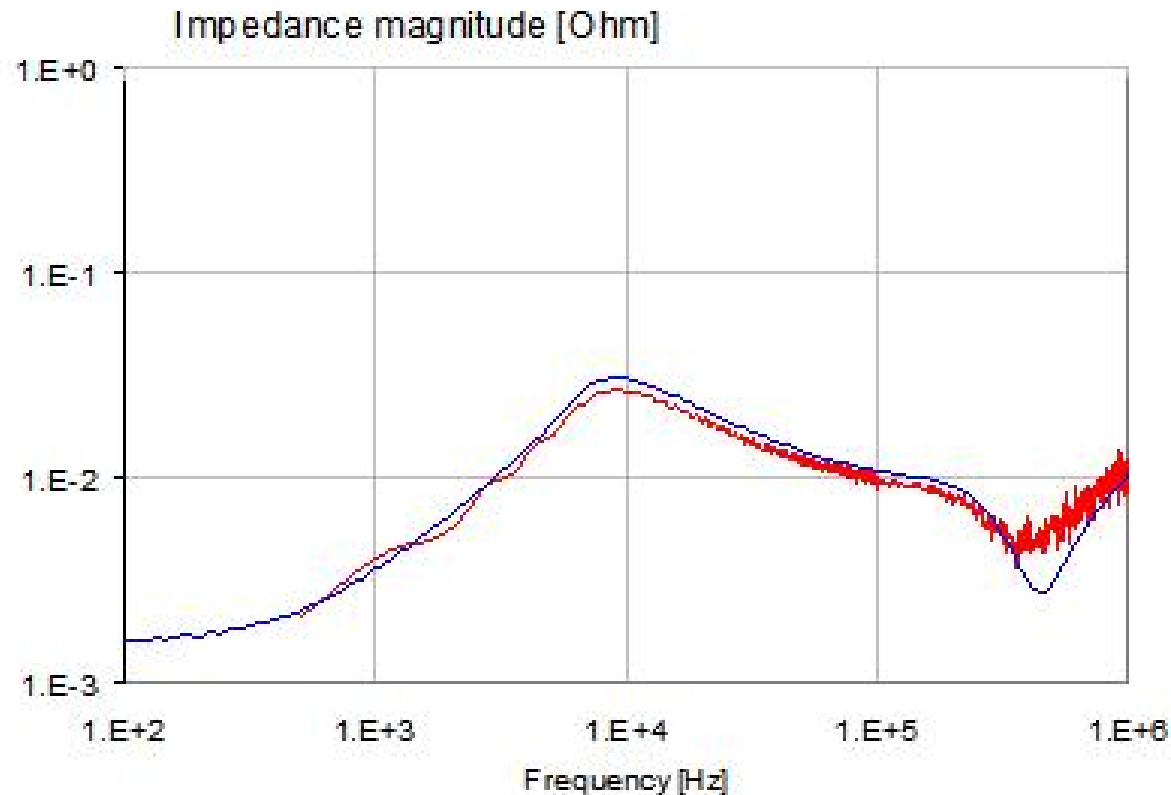

- Blue trace: small-signal Z_{out}
- Red trace: Z_{out} from Step Response




Conclusions

- **For linearized behavior**
 - Dynamic converter parameters can be based on the Gain-Phase function
 - Output impedance is a good measure for dynamic response
 - Output impedance can be measured or simulated by
 - Swept-sine small signal
 - Swept-sine large signal
 - Derivative of the Fourier Transform of the Step Response
 - Source impedance can greatly influence output impedance
 - Output impedance can go above OFF impedance (peaking) for several decades beyond the crossover frequency



Conclusions (continued)

- **Paralleled converter outputs will**
 - Reduce output impedance proportional to the number of phases
 - Not change crossover frequency
- **Nonlinear control can reduce the magnitude of instantaneous transient response**
- **Gain-Phase and output impedance measurements can be achieved with a unified setup**

 


Part II: Power Filter Network and its Effect on DC-DC Converters

Kendrick Barry Williams, Oracle-America Inc.

Istvan Novak, Oracle-America Inc.

Brandon Howell, Intersil Corporation

Chris Young, Intersil Corporation

 


Outline

Part II: Power Filter Network and its Effect on DC-DC Converters

 
• I. Introduction and Background Information

- DC Converters Introduction
- Power Filter Introduction
 - DC Converter Specifications
 - Filter Specifications
 - The DC Converter Application
 - Cross-Over Frequency



Outline (continued)

 - Power Filter Application
- Filter input impedance, converter looking toward the load
- Filter input impedance, the load looking toward the converter
- Filter Inductor
- **II. Actual Circuit Used and Measurements**
 - Added Bulk Capacitors Removed
- **Summary**




Outline

Part II: Power Filter Network and its Effect on DC-DC Converters

 
• I. Introduction and Background Information

- DC Converters Introduction
- Power Filter Introduction
 - DC Converter Specifications
 - Filter Specifications
 - The DC Converter Application
 - Cross-Over Frequency



Why Do We Need More Filtering?

 - I/O frequencies are increasing beyond 10Gb/s
- Sensitive circuits need reduced noise levels – less than 5 mV Pk – Pk
- Chips with PLL circuits operating at frequencies of 1 MHz and above




A Brief Survey – What Inductors Were Chosen?


- **Ferrite Beads for applications up to 6 Amperes**
- **Gapped Inductors for larger currents > 6 Amperes**
- **Need for low resistive loss to keep efficiencies high**
- **Small Size**

DESIGNCON 2012




WHERE CHIPHEADS CONNECT

 


Gapped Inductors

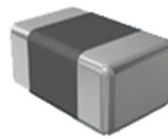

Ferrite Beads

   

UBM
Electronics

 


Important Things About Inductors

- **Signal Inductors are very sensitive to DC bias currents**
- **Power Line Ferrite Beads**

Resistive value decreases with increasing current


Inductance decreases with increasing current

 Not all ferrite beads are created equally!




Ferrite Bead DC Bias

 The effects of DC bias is dependent on the materials used in the manufacturing of the product




Ferrite Bead, 30 Ω
Red, DC Current = 0.0 A
Blue, DC Current = 1.8 A

 
Not all suppliers
provide DC Bias
Information!!



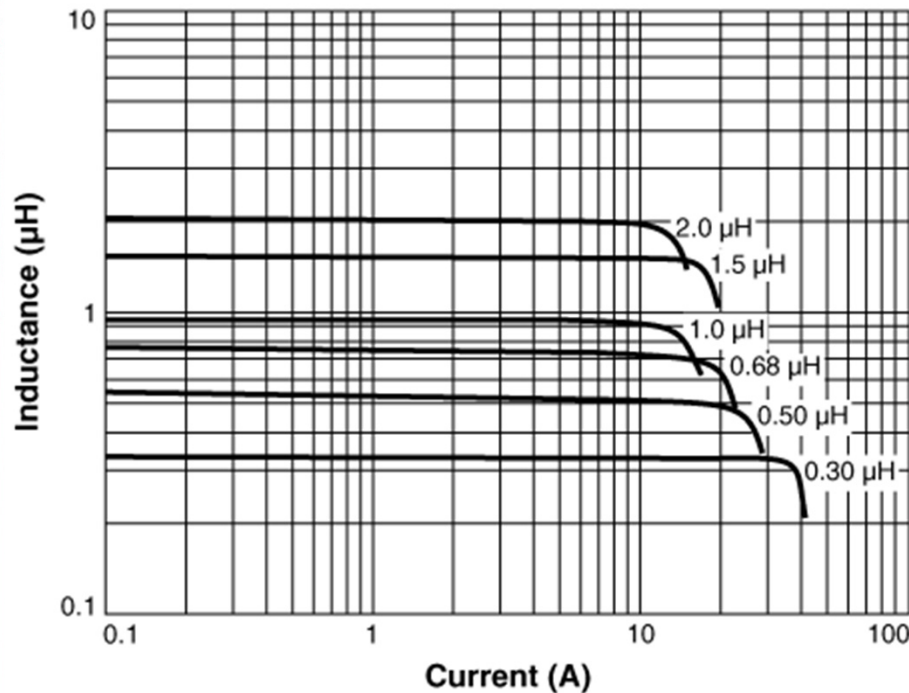We could of course use a big power inductor !!



 The larger inductors
behave more in
line with OUR
expectations




Power Supplies – Where is the Industry going?

Integrated Power Solutions

- **FETs and Inductor integrated with controller**
- **Compensation loops integrated with the package**
- **User adds voltage divider to set output voltage**


Digital Control Systems

 - **PID Controllers offer a means to alter the behavior through firmware instead of added components.**





DC Converters

 **Typical Buck Regulator
Non – Isolated 10 Amp
15 mm x 15 mm x 3.5 mm**



**What information do we
need to know about this
regulator?**


**Fully Integrated,
PID Control**

  

Converter Consists Of

- (2) Power FETs**
- (1) Power Inductor**
- (1) Digital Controller**

Basic DC Converter Implementation

 


The converter vendor does provide information about:

**Input Voltage Range
Output Voltage Range
Output Current
Switching Frequency
Line and Load
Regulation
Set Point Accuracy**

The converter vendor does not provide information about:

 
**Type of Controller:
Voltage Mode
Current Mode
Bandwidth of Loop
Compensation
Cross – Over Frequency
Output Inductor & DCR**






Filter Requirements, What are they?

 Vendors in general don't provide information on what the max noise voltage that can be tolerated, nor the frequency range needed



Attenuation Requirements ???

 

Filter Requirements – General Rule of Thumb

Remember!!!!

General Rules of Thumb
make certain assumptions
that may or may not be true!

Assumed Filter Requirements

Assumptions

1. Nominal Noise Voltage of 1mV
2. Attenuation -20dB/decade
3. Corner Frequency 100 KHz
And 100 MHz




DESIGNCON 2012

WHERE CHIPHEADS CONNECT




DC Converter—PDN

Big “V” PDN

 

Big “V” resulting from usage of many of the same capacitor


Flat Z PDN

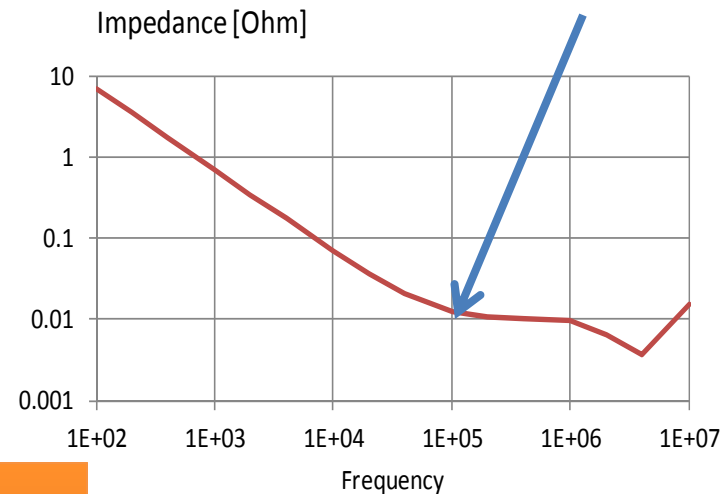

Flat Region resulting from several different types of capacitors

DESIGNCON 2012

WHERE CHIPHEADS CONNECT

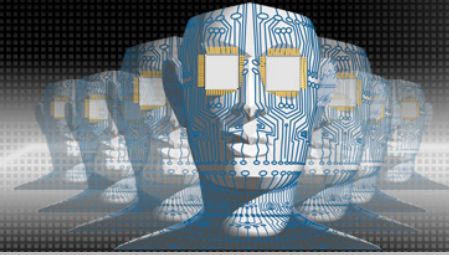

DC Converter — Target Impedance

Example



V_{out} = 1.800 V

I_{out} = 4.000 A

Set Point Accuracy = 18 mV

Max deviation = 90 mV (5%)

Inductor Ripple Current = 1.200 A

  


Allowances

90 mV – 18 mV = 72 mV

Ripple Voltage = 37.5% or 27 mV

Target Z = 27 mV / 1.200A = 22.5 mΩ

 

DC Converter Loop Cross – Over Frequency Problem


Issues:

An integrated regulator.

No information about the internal inductor.

No information on the type of controller.

 
No information about the loop compensation



Solutions:

Ask the vendor or....

 Assume both Voltage Mode and
Current Mode Controller



Estimating The Cross – Over Frequency For a Current Mode Controller

Estimated Corner Frequencies

$$F_{c1} = 1 / (\omega R_{load} C_{bulk})$$

$$F_{c2} = 1 / (\omega R_{ESR} C_{bulk})$$

Estimated Gain Needed

$$\text{Gain Needed} \sim 10^{((120 - G) / 20)}$$


$$\text{Where } G = 20\text{Log}(V_{out} / V_{ripple})$$


Estimated Error Amplifier Gain

0 dB @ 1 MHz

+ 120 dB @ 1 Hz.


Error Amp Gain (dB)

 

 


Power Filter Application – What is it that we need to Accomplish?

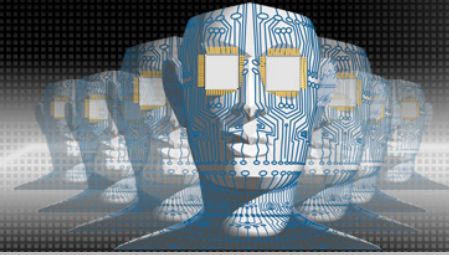- **Just as in Signal Integrity work, we need to match the load to the source.**
- **We also must match the source to the load.**
- **We need to have sufficient attenuation to meet the requirement of the target device, without gain.**
- **We shall not cause instability of the regulator with the additional filter.**




Matching the Source to the Load

 


DESIGNCON 2012


WHERE CHIPHEADS CONNECT

 

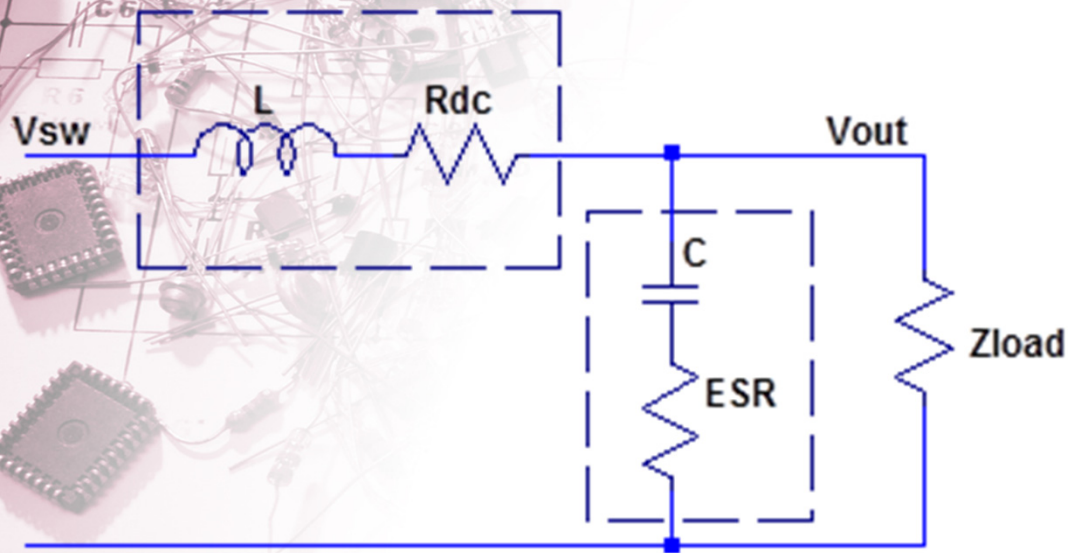What the Regulator Will See With a Filter




=


 


DESIGNCON 2012


WHERE CHIPHEADS CONNECT

 


What Will The Load See?

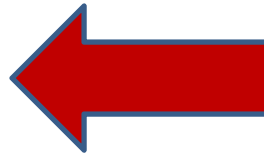 

The Load
Sees Just
the PDN

 


What The Load Sees With A Filter

 

**Do We Have a Nasty
Parallel Resonance
Problem ?**

DESIGNCON 2012

WHERE CHIPHEADS CONNECT

 

Parallel Resonance – Defining Its Value

Isn't its frequency just


$$Fr = \frac{1}{\omega\sqrt{LC}}$$

Actually, it is more than that

$$Fr = \frac{1}{\omega\sqrt{LC}} \sqrt{1 - \frac{CR^2}{L}}$$


And if the radical is set to “0”, then there is no resonance!!

Suggesting that ... $\frac{1}{Q} = RY_o$

 

Outline (continued)

 - Power Filter Application
- Filter Input Impedance, converter looking toward the load
- Filter Output Impedance, the load looking toward the converter
- **II. Actual Circuit Used and Measurements**
 - Added Bulk Capacitors Removed
- **Summary**



DESIGN EXAMPLE -- 1

Design Requirements # 1:

Ripple and Noise Voltage 1 mV @ Load
Attenuation Profile

-20dB starting at 100 KHz

+20 dB starting at 10 MHz

Ripple Voltage from regulator27 mV

Target Impedance 22.5 m Ω

PDN – Flat Impedance Design

(1) 220 μ F, Poly. Tant. ESR = 25 m Ω

(1) 22 μ F, Ceramic, 10 V, X5R ESR = 4 m Ω

(1) 2.2 μ F, Ceramic, 10 V, X5R ESR = 10 m Ω



DESIGNCON 2012

WHERE CHIPHEADS CONNECT



DESIGN EXAMPLE -- 2

Design Requirements # 2:

Ripple and Noise Voltage 1 mV @ Load
Attenuation Profile

-20dB starting at 100 KHz

+20 dB starting at 10 MHz

Ripple Voltage from regulator27 mV

Target Impedance 22.5 m Ω

PDN – Big “V”


(1) 22 μ F, Ceramic, 10 V, X5R ESR = 4 m Ω



UBM
Electronics

DESIGNCON 2012


WHERE CHIPHEADS CONNECT

 

DESIGN EXAMPLE -- 3

Regulator Specifications:

 1. Switching Frequency..... 1 MHz
2. Controller Type Current Mode (Asked Vendor)
3. Set Voltage 1.800 V
4. Output Current 4.0 A
5. Minimum Bulk Capacitance ...22 μ F



Error Amp Cross – Over Frequency Estimation

$$\text{Gain Needed} = 20\text{Log}(V_{\text{out}} / V_{\text{ripple}}) = 32.64 \text{ dB}$$

$$F_{c1} = 1/(2\pi(0.45)(22 \mu\text{F})) = 16.1 \text{ KHz}$$

$$F_{c2} = 1/(2\pi(0.004)(22 \mu\text{F})) = 1.81 \text{ MHz}$$


$$F_{0\text{dB}} = ((F_{c1})(F_{c2}))^{0.5} = 170 \text{ KHz}$$

$$F_{c1} = 1/(2\pi(0.45)(242 \mu\text{F})) = 1462 \text{ Hz}$$


$$F_{c2} = 1/(2\pi(0.002)(242 \mu\text{F})) = 329 \text{ KHz}$$

$$F_{0\text{dB}} = ((F_{c1})(F_{c2}))^{0.5} = 22 \text{ KHz}$$

Gain (22 uF) [dB]

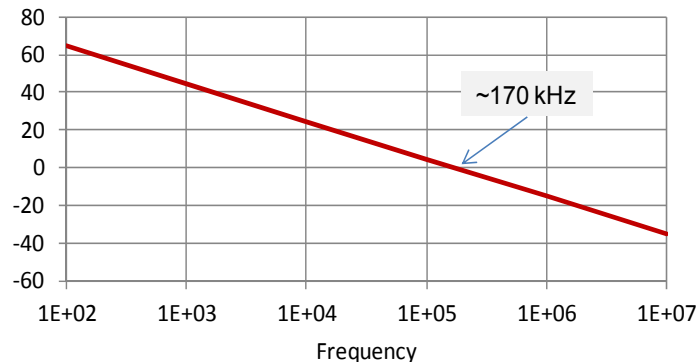


Gain (242 uF) [dB]

 





Regulator OFF, Quick Estimates of PDN Impedance, Cross – Over Frequency, and Target Impedance

Case #1 Bulk C = 242 μ F

 

Case #2 Bulk C = 22 μ F

 

 

Filter Design

Looking From Converter to Load


Attenuation Needed is base on -20 dB/decade

Ripple Voltage = 27 mV,
(Maximum Noise Voltage)(0.5)/Ripple Voltage = -34.6 dB

Specified attenuation to occur at 1 MHZ; therefore,
Corner Frequency = $(1 \text{ MHz})(10^{(\text{Attenuation}/20)}) = 13\text{KHz}$

Initial value of Inductance = $\text{Target } Z/(\omega F_{\text{corner}}) = 274 \text{ nH}$

 Initial value of Capacitance = $\text{Inductance}/(\text{Target } Z)^2 = 540 \text{ }\mu\text{F}$



Filter Design Continued

Our survey indicated a need for small parts.

With an inductance value of 274 nH in a ferrite bead rated for our maximum current of 4 Amps is tough to get.

Lowered the value of inductance to 120 nH which is readily available and is small, 0603 package.

In lowering the inductance, the capacitance needs to be valued, the new value based on the Z_0 of the filter suggests a value of 270 μF , 220 μF has been selected, a poly Tantalum, $\text{ESR} = 25 \text{ m}\Omega$.

To extend the bandwidth, (2) 22 μF ceramic capacitors were added.



DESIGNCON 2012

WHERE CHIPHEADS CONNECT




How well did we do?


Met the corner frequency requirement

Virtually NO Gain!

Met the Attenuation factor at 1 MHz

Filter Characteristics

 

 

Filter Design Continued


From The Load Side, Looking Toward The Regulator

The requirement is that the load should see the PDN at the regulator, this value is $22.5 \text{ m}\Omega$. We chose a $25 \text{ m}\Omega$ poly tantalum capacitor which is sufficient in terms of the ESR of the capacitor.

However, the tantalum capacitor turns inductive at about 1 MHz , it needs to be countered with ceramic capacitors that will extend the attenuation bandwidth towards 10 MHz .

DESIGNCON 2012


WHERE CHIPHEADS CONNECT

 

Total Design Solution


Filter Characteristics

Z11, Z22, Attenuation

 

Green,
looking from
the load to the
converter.

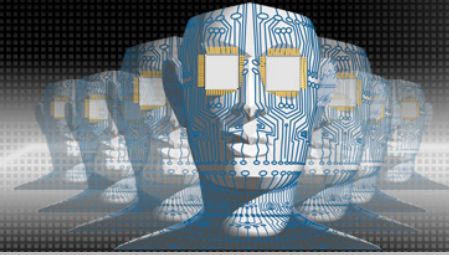Red,
looking from
the converter
to the load



Measurements


Measurements in the following section, were done with the filter added


Added Filter

Current Mode Controller

Regulator Evaluation Board

Bulk Capacitance added

 


 


Measured Output PDN – Case # 1

Regulator OFF


Regulator ON, 0 Ampere Load

Cross – Over Frequency Regulator

  



DESIGNCON 2012

WHERE CHIPHEADS CONNECT

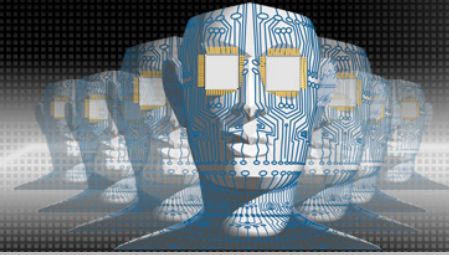

Measured Ripple Voltage

 


 



Measured Output PDN – Case # 2

Regulator OFF


Regulator ON, 0 Ampere Load


Cross – Over Frequency Regulator

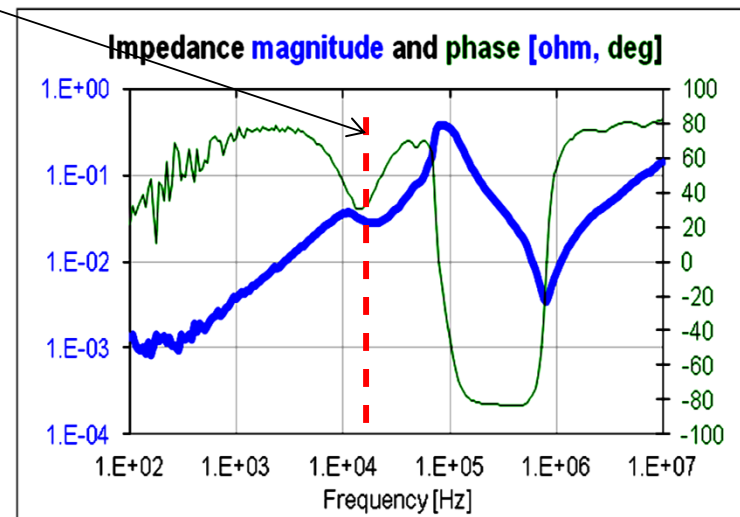 

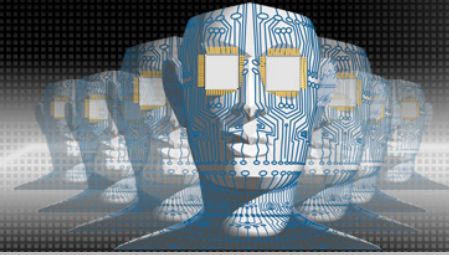


Measured Ripple Voltage Case #2

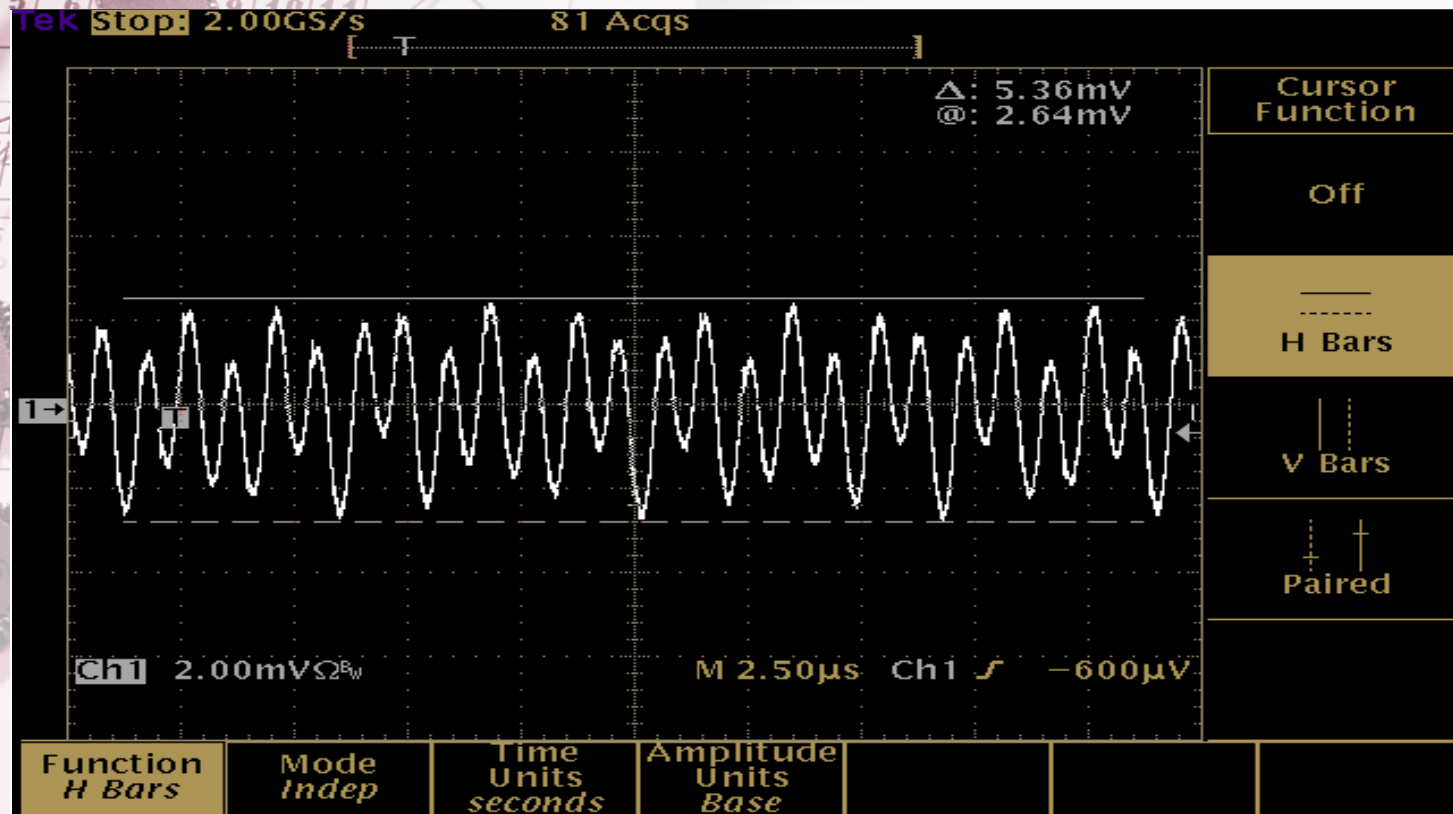

 



Comparison Of Measured Output PDN Case # 1 & # 2

Regulator OFF, Case # 1

 


Regulator OFF, Case # 2

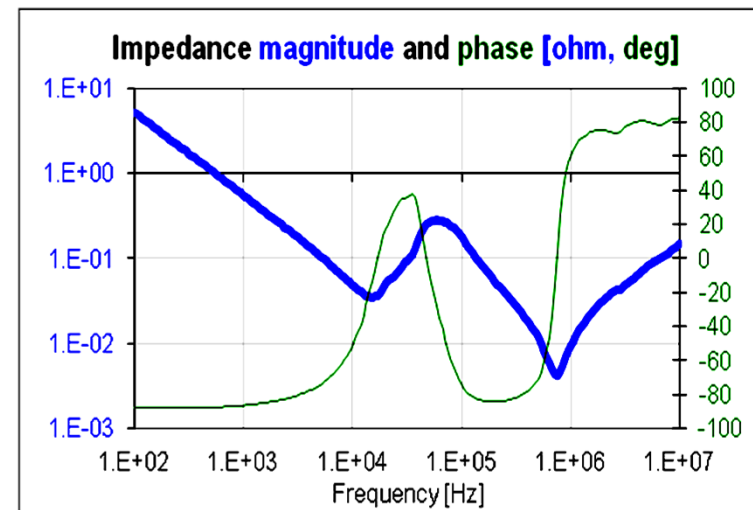

 



Comparison Of Measured Output PDN Case # 1 & # 2

Regulator OFF, Case # 1

 


Regulator OFF, Case # 2

 

 


Comparison Of Measured Output PDN Case # 1 & # 2

Regulator ON, 0 Ampere, Case # 1

 

Regulator ON, 0 Ampere, Case # 2

 




Attenuation Measurements


Case # 1, 0 Ampere Load

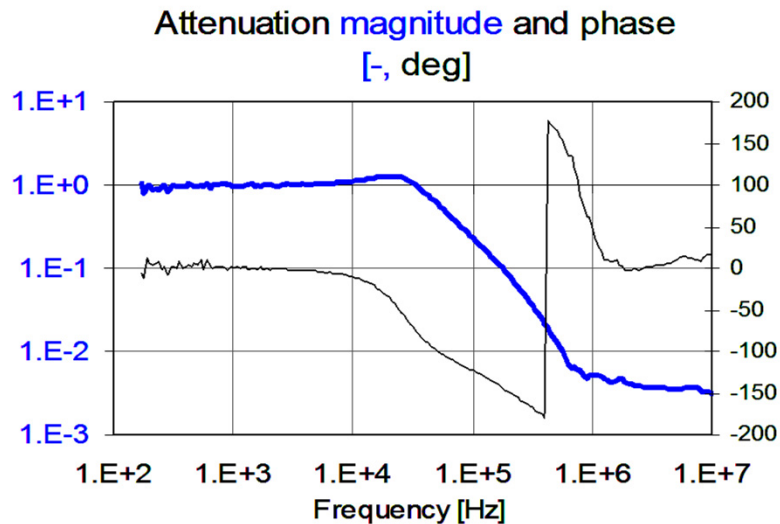
Filter appears to have a slight lift, and the corner frequency is about 30 KHz, somewhat higher than simulation results.



Case # 1, 4 Ampere Load

 
Filter Inductance appears to have dropped by a factor of about 4, shows that the ferrite bead is affected by DC bias current.



 



Measured Ripple Voltage Before /After the Filter, 4 Amp Load

Ripple Voltage Before Filter

 

Ripple Voltage After Filter

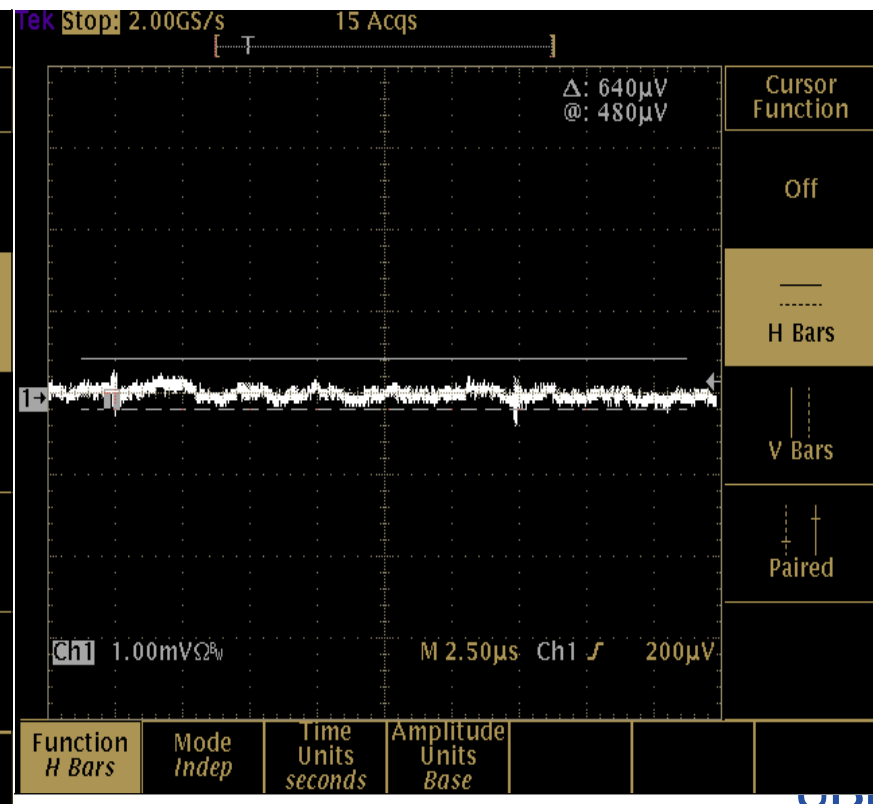

 

Moving The Converter Sense Lines


All the measurements made thus far, have the sense lines connected at the filter.

What if we move the sense lines to a point after the filter components, would we see any difference in performance?




Investigation of the movement of the sense lines begins by first looking at the output impedance of the regulator, that is at the bulk capacitors.

Regulator OFF

 

Regulator ON, 0 Ampere Load

 





Comparative Output Impedance, Before / After Sense Line Change


Regulators OFF

Sense Lines Before Filter

 

Sense Lines After Filter

 


 


Comparative Output Impedance, Before / After Sense Line Change


Regulators ON

Sense Lines Before Filter

 

Sense Lines After Filter

 


 


Comparative Output Impedance, Before / After Sense Line Change

Regulators ON, 4 Amp Load

Sense Lines Before Filter

Sense Lines After Filter

  





Comparative Attenuation, Before / After Sense Line Change

Attenuation, 4 Amp Load

Sense Lines Before Filter

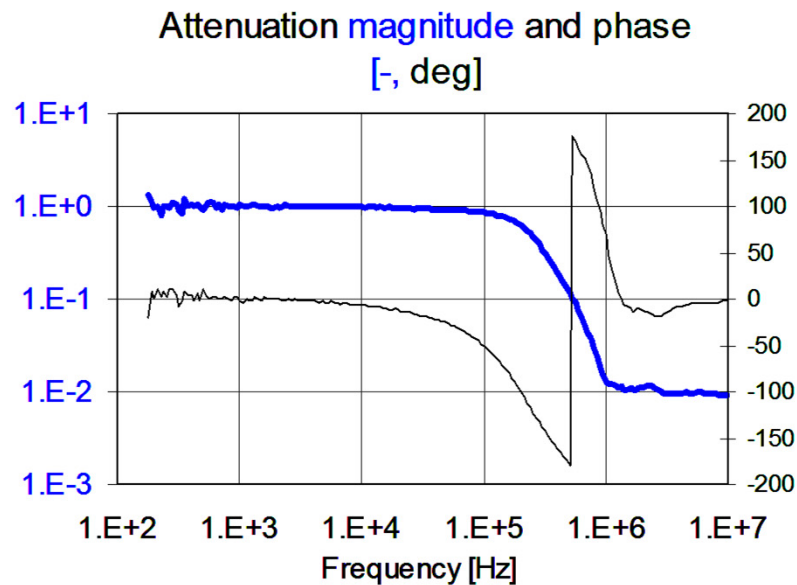

Sense Lines After Filter

 

DESIGNCON 2012


WHERE CHIPHEADS CONNECT




Comparative Attenuation, Before / After Sense Line Change


Ripple Voltage Attenuation, 4 Amp Load

Sense Lines Before Filter

 

Sense Lines After Filter

 

 


Change to Case #2, where the Bulk Capacitor is 22 μ F.
A comparison of the location of the sense lines, before and after the filter.

What are differences in Output Impedances with the change in the sense line location?


Is there any differences in Attenuation?

 Is there any differences in the measured ripple voltages?




Comparison of Output Impedances

Regulator OFF, Before Filter

 

Regulator OFF, After Filter


 




Comparison of Output Impedances

Regulator ON, 0 Amp Load, Before Filter

Regulator ON, 0 Amp Load, After Filter

 
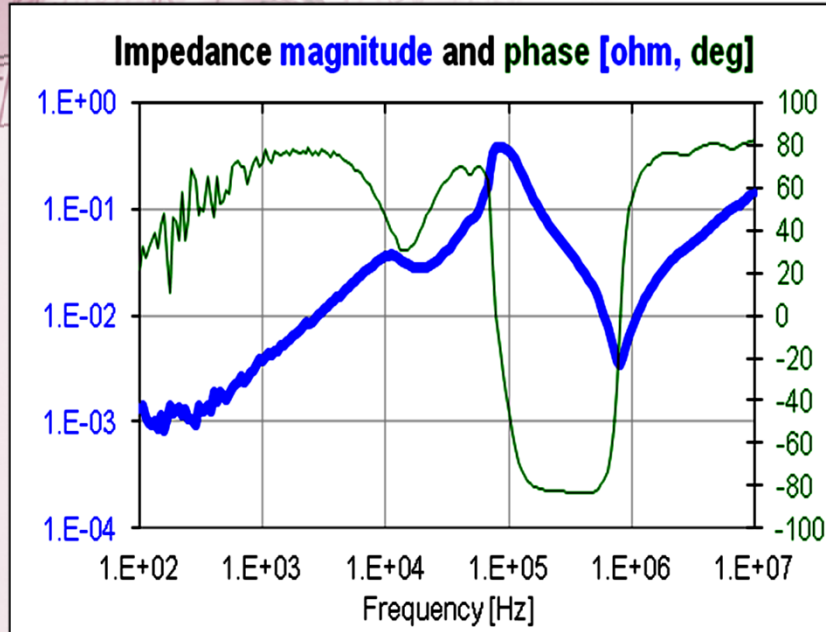





Comparison of Output Impedances

Regulator ON, 4 Amp Load, Before Filter


Regulator ON, 4 Amp Load, After Filter

  

 

Measured Attenuation With 0 Ampere Load

Attenuation magnitude and phase
[-, deg]

 

Some Strange
event going on
here!

DESIGNCON 2012



WHERE CHIPHEADS CONNECT




Comparison of Ripple Voltages

Regulator ON, 0 Amp Load, Before Filter


Regulator ON, 0 Amp Load, After Filter

  

 

Measured Attenuation With 4 Ampere Load

Attenuation magnitude and phase
[-, deg]

 



Here it is
again!




Comparison of Ripple Voltages

Regulator ON, 4 Amp Load, Before Filter


Regulator ON, 4 Amp Load, After Filter

 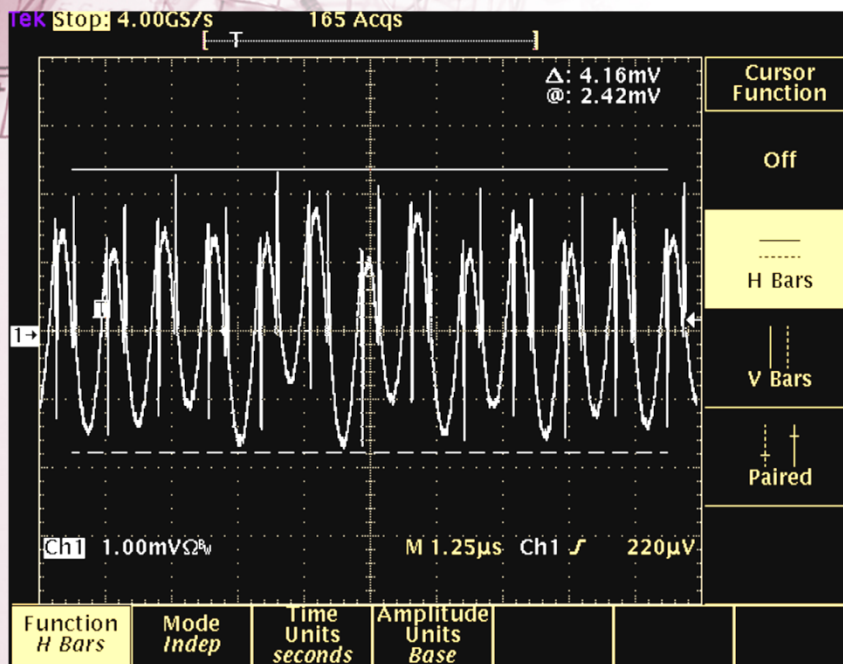

 


Summary of the Design Challenge

- Using a Current Mode Controller, without knowledge of any information about the compensation loop, we designed a power filter network that required a 1 mV noise level at 1 MHz.
- The resulting design using a target impedance that is basically flat;
 - The corner frequency of the filter occurs approximately where the simulation indicated
 - The resulting attenuation of the ripple noise was below the maximum assumed level required of 1 mV. Typical results show 500 – 800 μ V of noise voltage.
 - The DC converter showed no ill effect from having a power filter attached, it appears to be stable, indicating:
 - Matching the source to the load was accomplished
 - Matching the load to the source was also accomplished

 

Summary Continued – Surprises!

- Observation of the effects of a ferrite bead used to it maximum rated value of current indicates that the bead saturates, reducing its inductance and series resistance significantly.
- Use of a ferrite bead may cause the attenuation requirements not to be met even with a flat output impedance.
- Use of a target impedance that is constructed by using the concept of a Big “V”, with minimal amount of capacitance can be a significant problem.
 - It may cause instability of the DC converter.
 - Attenuation requirements may not be met.
- Sense lines for the DC converter should be located before the filter to avoid instability issues for the DC converter.

 

Other Observations

- In the design of the power filter, the corner frequency should be higher in frequency than the cross – over frequency of the compensation loop.
- There will be no interference between the 2 systems, the compensation loop does not necessarily maintain the output impedance beyond the point where the gain goes below 0 dB.
- Using a corner frequency inside the compensation loop control may alter the phase and should it fall so that there is no phase margin, may cause instability issues for the DC converter.
- Placing the sense lines of the converter before the filter helps to avoid the issue of interference between the 2 systems.



THANK YOU!

ANY QUESTIONS?