

Overview and Comparison of Power Converter Stability Metrics

Joseph 'Abe' Hartman, Oracle
Alejandro 'Alex' Miranda, Oracle
Kavitha Narayandass, Oracle
Alexander Nosovitski, Oracle
Istvan Novak, Oracle




SPEAKERS



Joseph 'Abe' Hartman

Principle Hatrdware Engineer, Oracle
abe.hartman@oracle.com | www.oracle.com

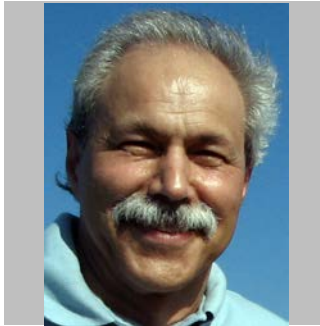

Istvan Novak

Senior Principle Hatrdware Engineer, Oracle
istvan.novak@oracle.com | www.oracle.com



Agenda

- Introduction
- Gain-phase plots
 - Traditional gain-phase plots
 - Gain-phase plot approximations and non-invasive measurements
- Nyquist plots and Stability margin
- Other metrics
- What can go wrong?
 - Wrong test signal level
 - Spurious signals
 - Impact of test equipment and load circuit
 - Measurement location
- Summary and Conclusions




Agenda

- Introduction
- Gain-phase plots
 - Traditional gain-phase plots
 - Gain-phase plot approximations and non-invasive measurements
- Nyquist plots and Stability margin
- Other metrics
- What can go wrong?
 - Wrong test signal level
 - Spurious signals
 - Impact of test equipment and load circuit
 - Measurement location
- Summary and Conclusions




Basic Buck Converter and its Loop Model

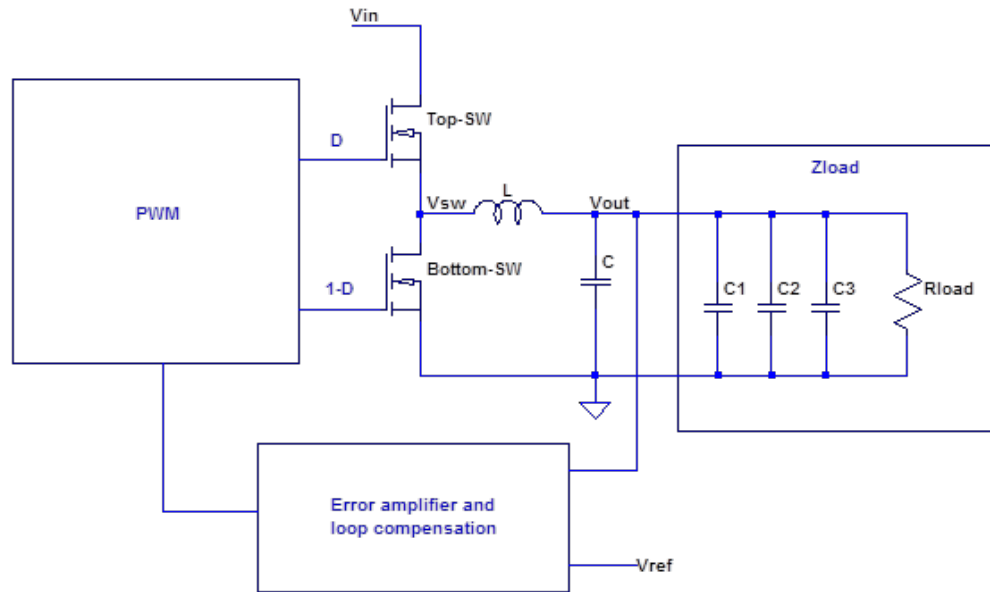Non-isolated buck converter block schematic



Simplified feedback loop

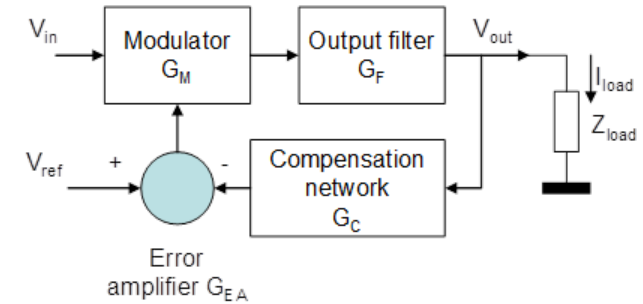


$$G_{open-loop} = G_M G_F G_C G_{EA}$$



Bode Plot, Phase and Gain Margins

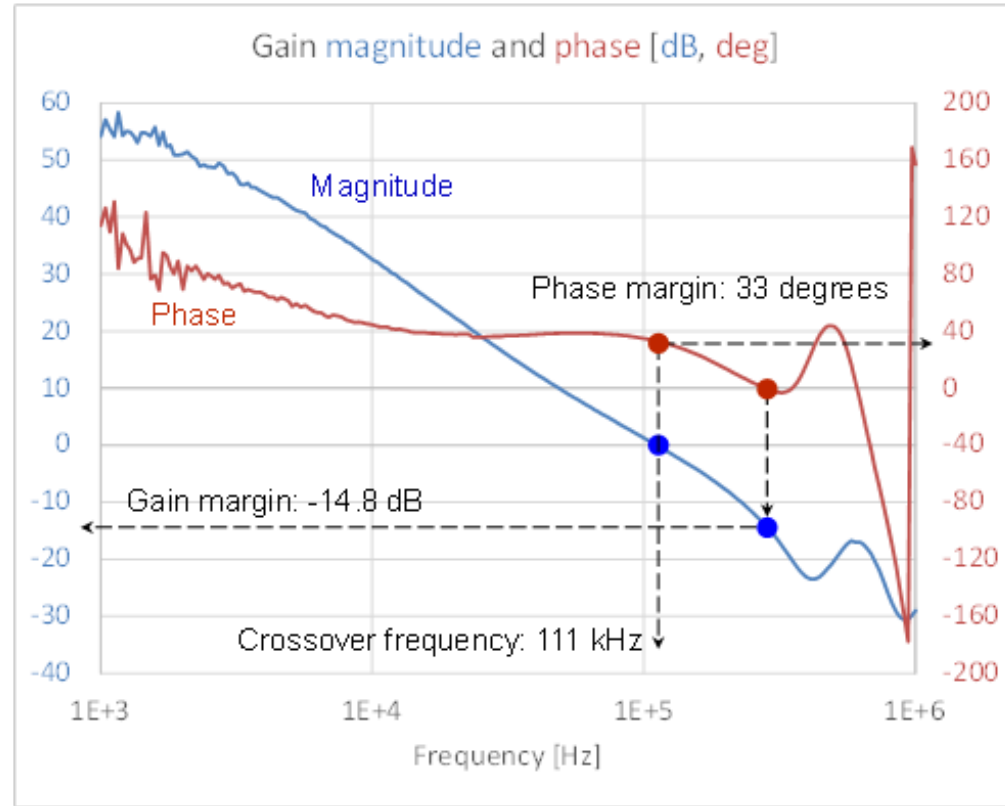
- Crossover Frequency – frequency where gain magnitude equals 0 dB
- Phase Margin – phase at the crossover frequency
- Gain Margin – gain where phase equals 0 degrees



Nyquist Plot

- Plots imaginary vs. real component of loop gain
- Frequency parameter
- Point of instability is -1,0

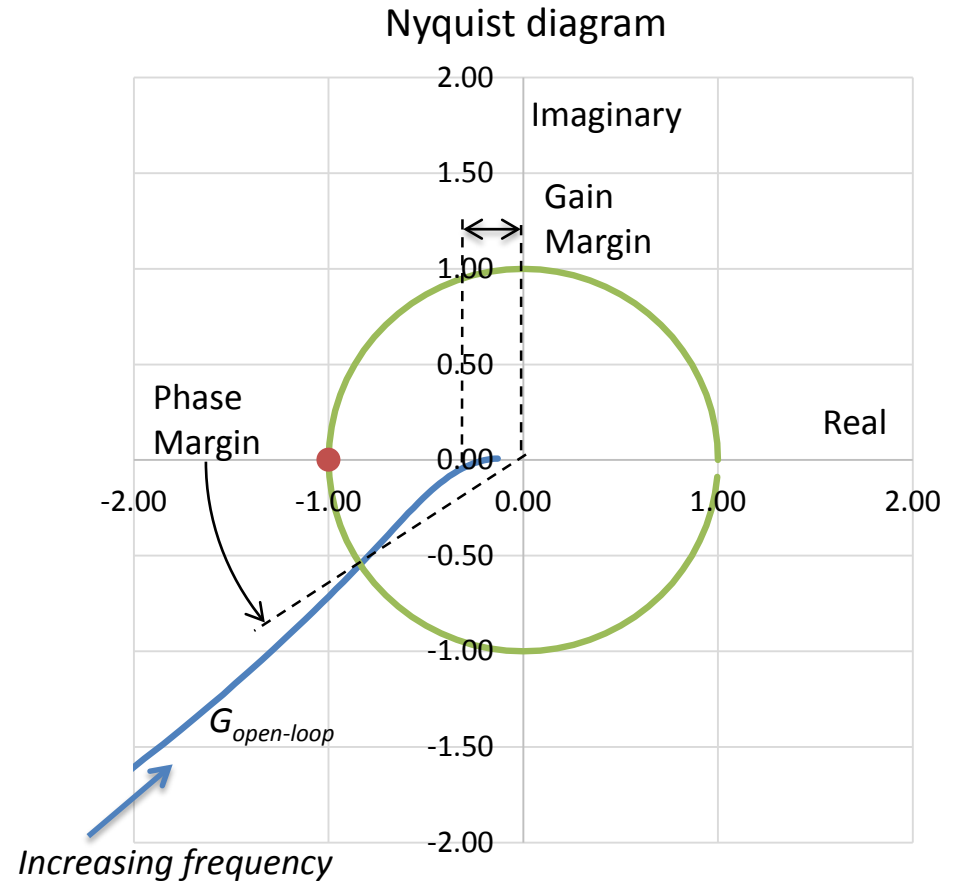
$$\frac{\Delta V_{out}}{\Delta I_{load}} = Z_{out-closed-loop}(f) = \frac{Z_{out-open-loop}(f)}{1 + G_{open-loop}(f)}$$



Characteristic Expression Magnitude and Its Inverse

- Plots $\{1+G_{open-loop}(f)\}$ and its inverse, the stability margin
Provides the vector magnitude from the instability point

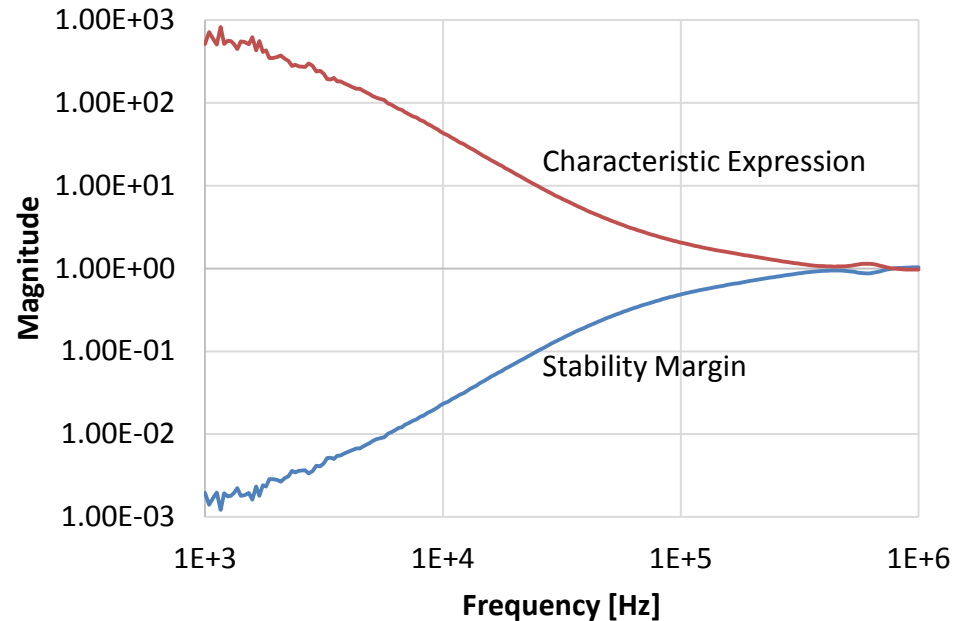Characteristic expression and its inverse
[-]




Agenda


- Introduction
- Gain-phase plots
 - Traditional gain-phase plots
 - Gain-phase plot approximations and non-invasive measurements
- Nyquist plots and Stability margin
- Other metrics
- What can go wrong?
 - Wrong test signal level
 - Spurious signals
 - Impact of test equipment and load circuit
 - Measurement location
- Summary and Conclusions



Gain-Phase Measurement Connection

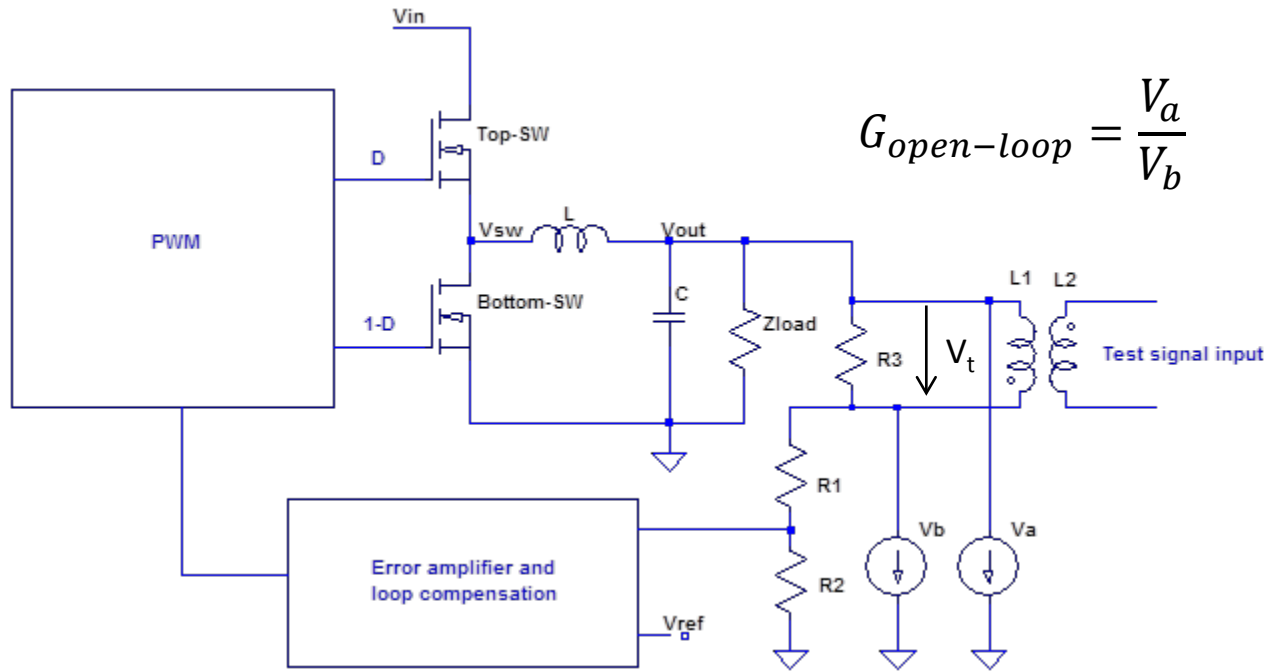

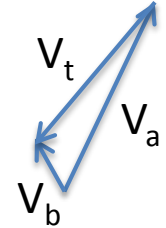- Requires floating source
- Injection level is important
- Invasive connection



Agenda




- Introduction
- Gain-phase plots
 - Traditional gain-phase plots
 - Gain-phase plot approximations and non-invasive measurements
- Nyquist plots and Stability margin
- Other metrics
- What can go wrong?
 - Wrong test signal level
 - Spurious signals
 - Impact of test equipment and load circuit
 - Measurement location
- Summary and Conclusions



Gain-Phase Measurement Based on Impedance (1)

- Open-loop output impedance can be approximated by OFF impedance
- 'Peaky' example
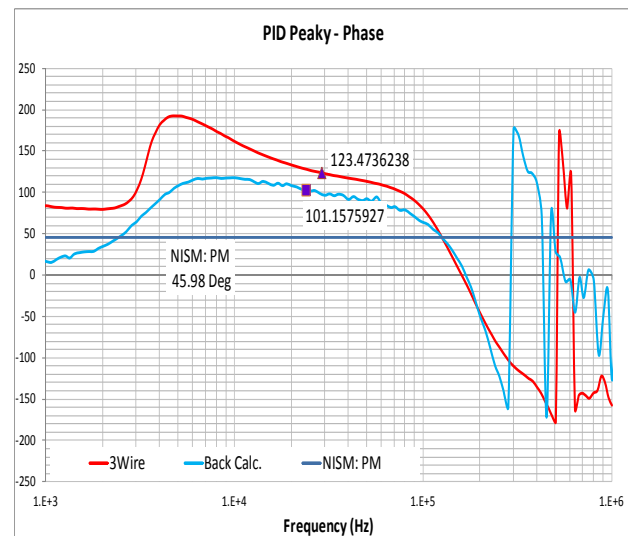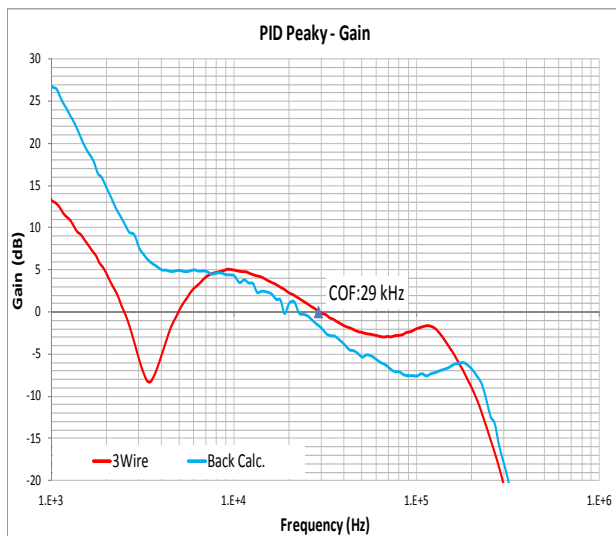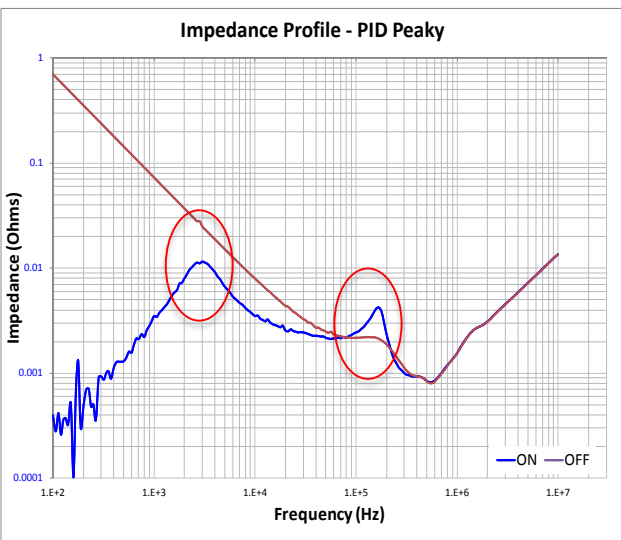
$$G_{open-loop}(f) = \frac{Z_{out-open-loop}(f)}{Z_{out-closed-loop}(f)} - 1$$






Steve Sandler, "Killing the Bode Plot," DesignCon 2016, January 19-21, 2016, Santa Clara, CA.



Gain-Phase Measurement Based on Impedance (2)

- Open-loop output impedance can be approximated by OFF impedance
- Optimized example
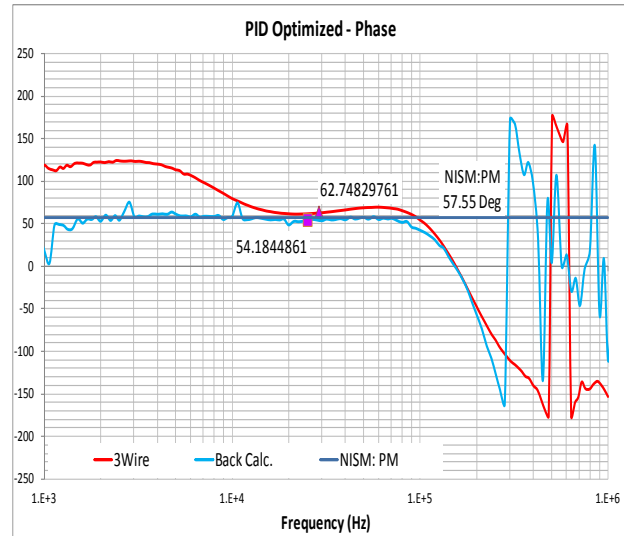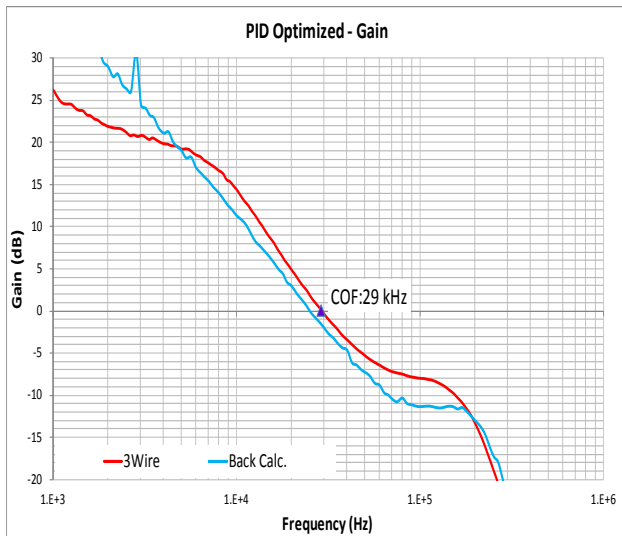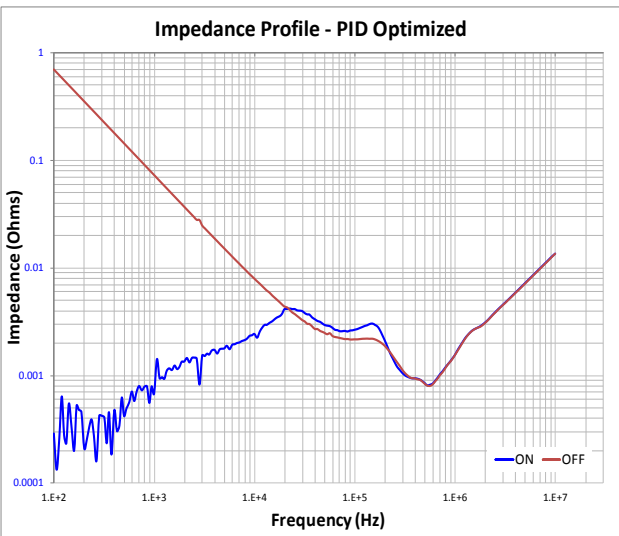
$$G_{open-loop}(f) = \frac{Z_{out-open-loop}(f)}{Z_{out-closed-loop}(f)} - 1$$





Steve Sandler, "Killing the Bode Plot," DesignCon 2016, January 19-21, 2016, Santa Clara, CA.




Gain-Phase Measurement Based on Impedance (3)

- DC bias for OFF impedance is important

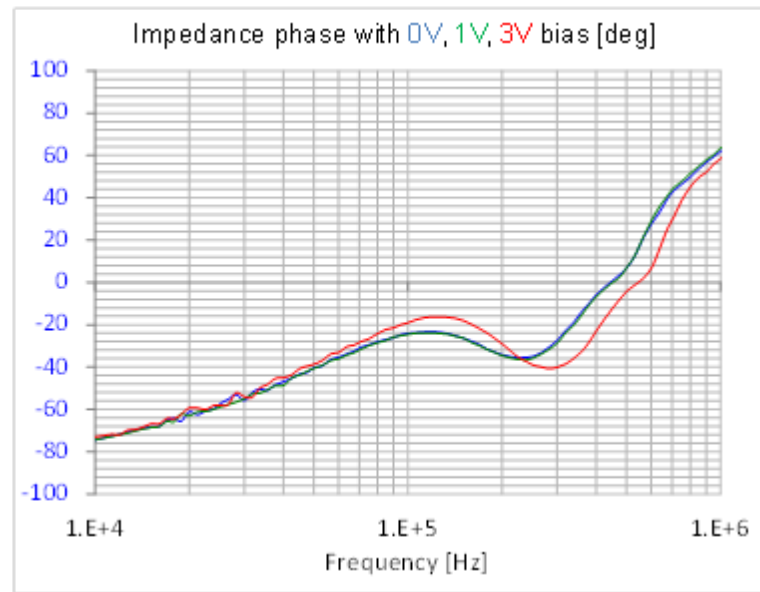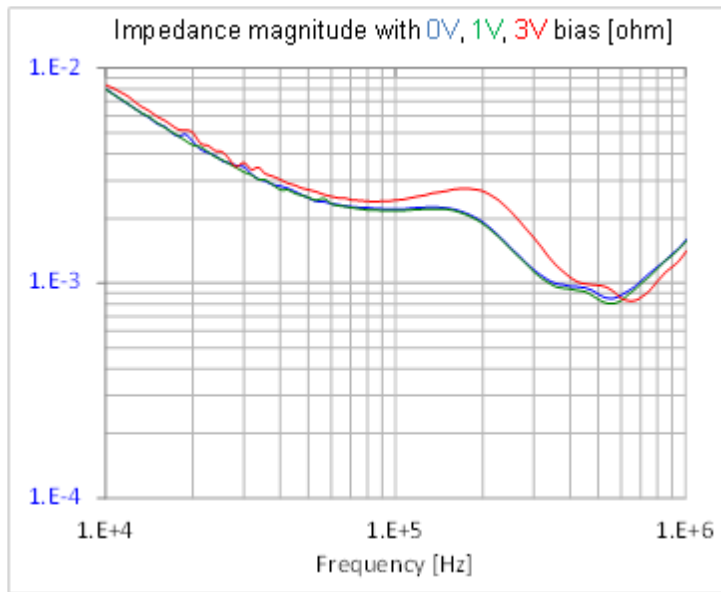

NISM Example on Low-Noise DUT

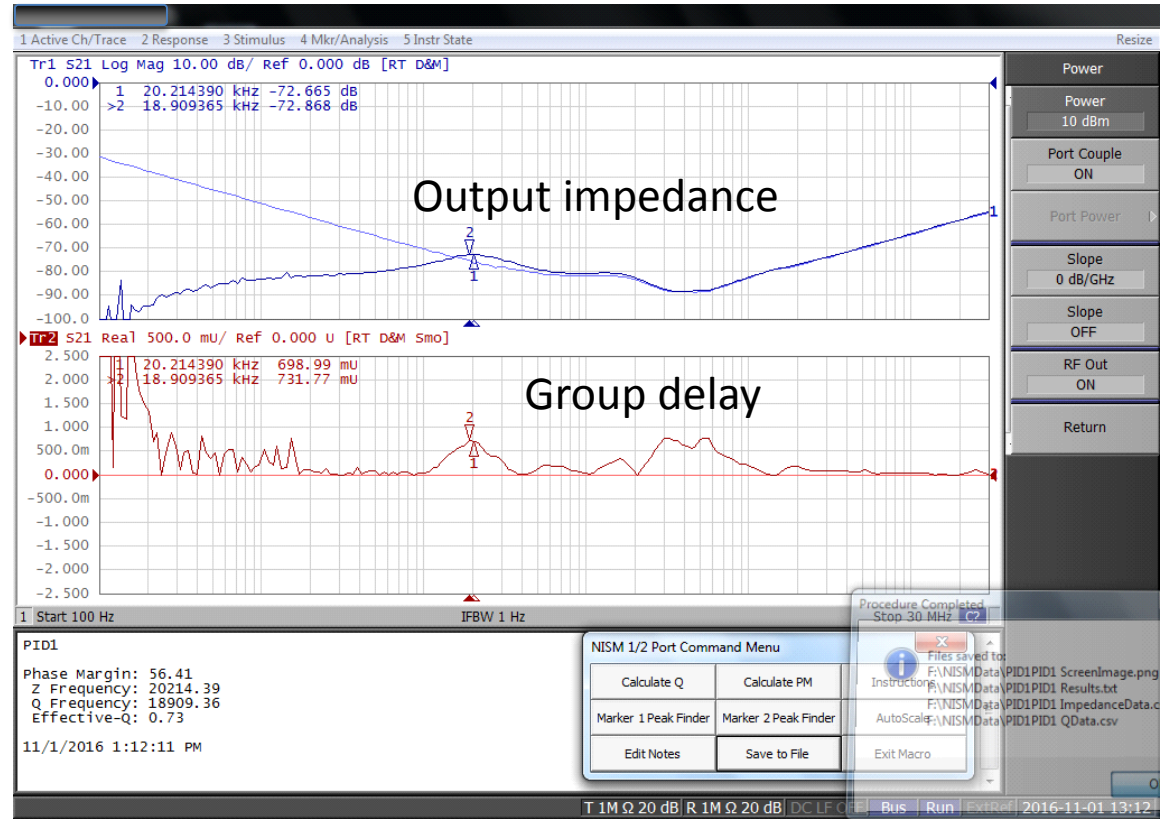- NISM is noninvasive
- Estimates phase margin based on second order model of output impedance




Steve Sandler, "Killing the Bode Plot," DesignCon 2016,

January 19-21, 2016, Santa Clara, CA.



NISM Example on High-Noise DUT

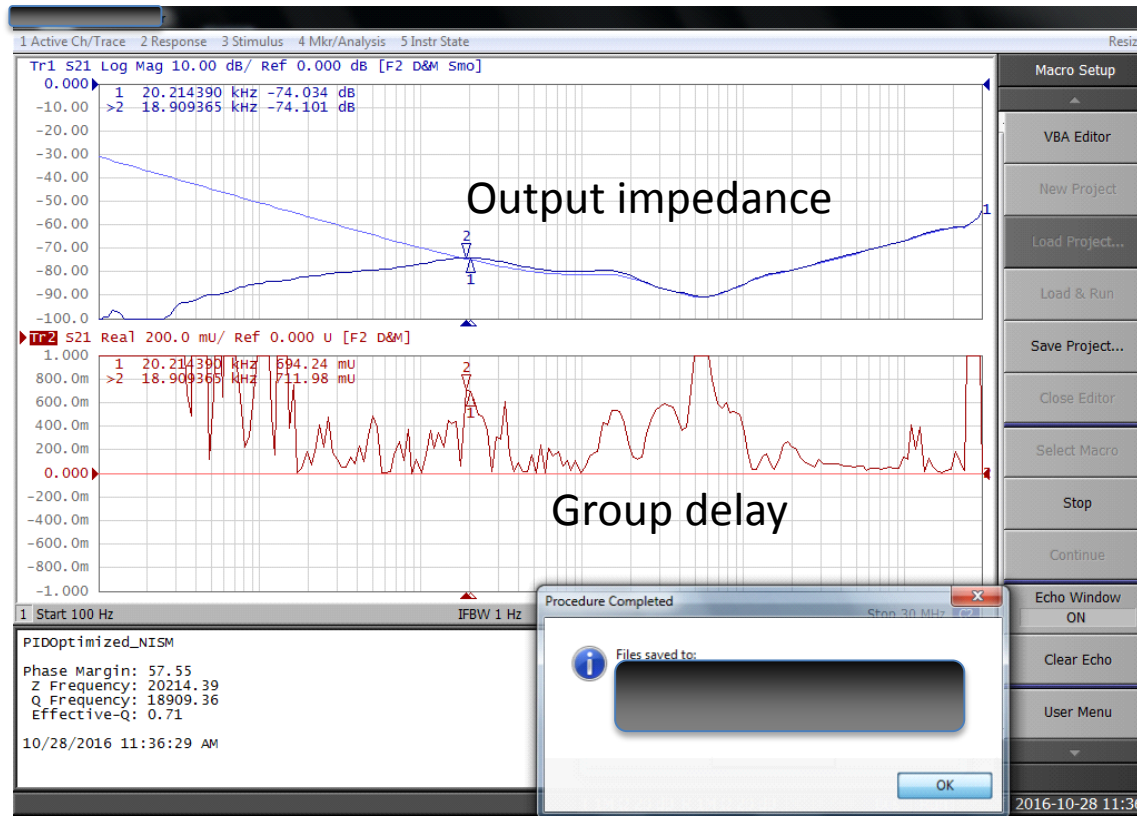

Steve Sandler, "Killing the Bode Plot," DesignCon 2016, January 19-21, 2016, Santa Clara, CA.




Agenda

- Introduction
- Gain-phase plots
 - Traditional gain-phase plots
 - Gain-phase plot approximations and non-invasive measurements
- Nyquist plots and Stability margin
- Other metrics
- What can go wrong?
 - Wrong test signal level
 - Spurious signals
 - Impact of test equipment and load circuit
 - Measurement location
- Summary and Conclusions




Impedance, Gain-Phase on Unstable Converter

Impedance magnitude ON, OFF [ohm]

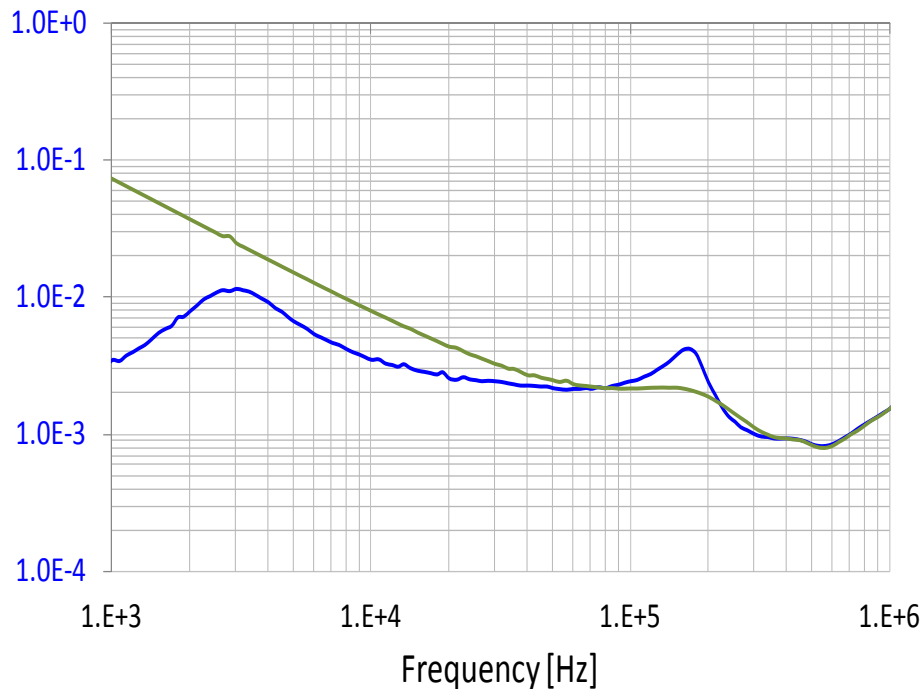


Measured gain magnitude, phase [dB, deg]

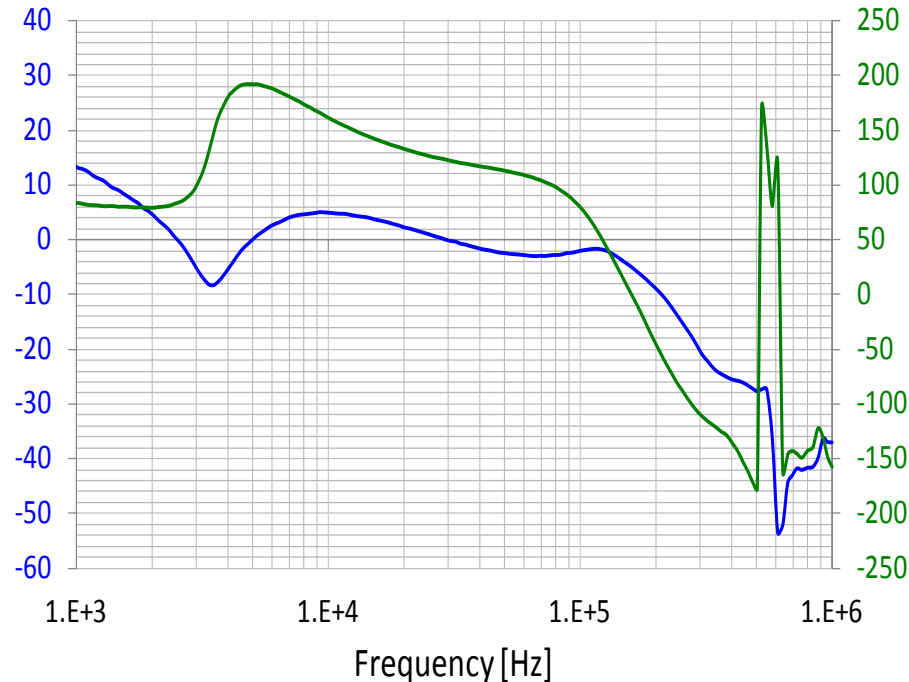


Nyquist and Stability Plots on Unstable Converter

Nyquist Plot

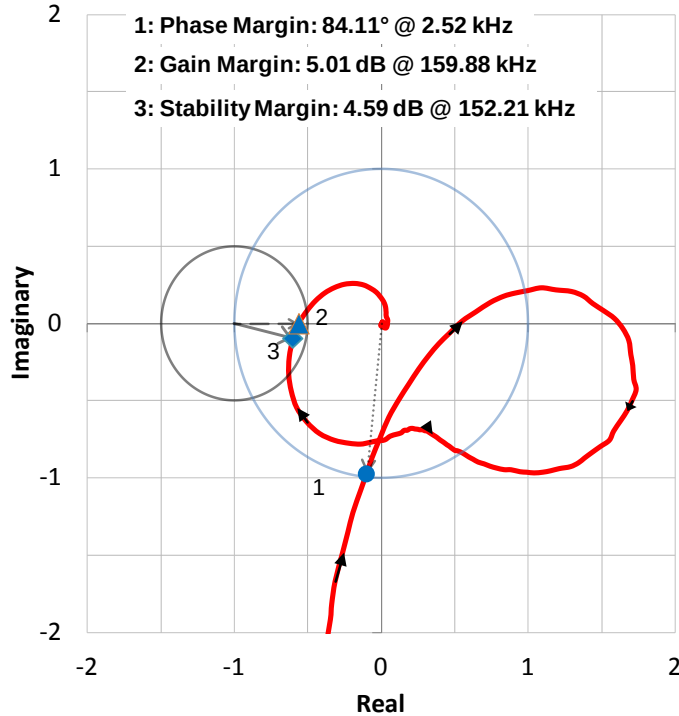


Characteristic Equation

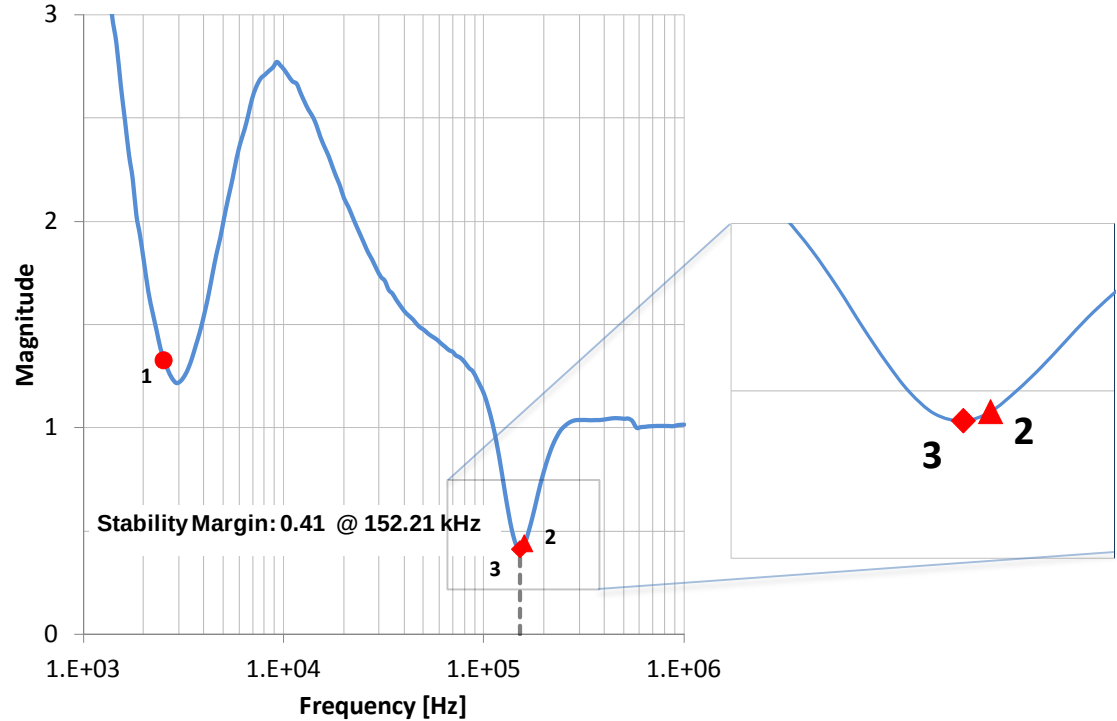


Impedance, Gain-Phase on Stable Converter

Impedance magnitude, ON, OFF [ohm]

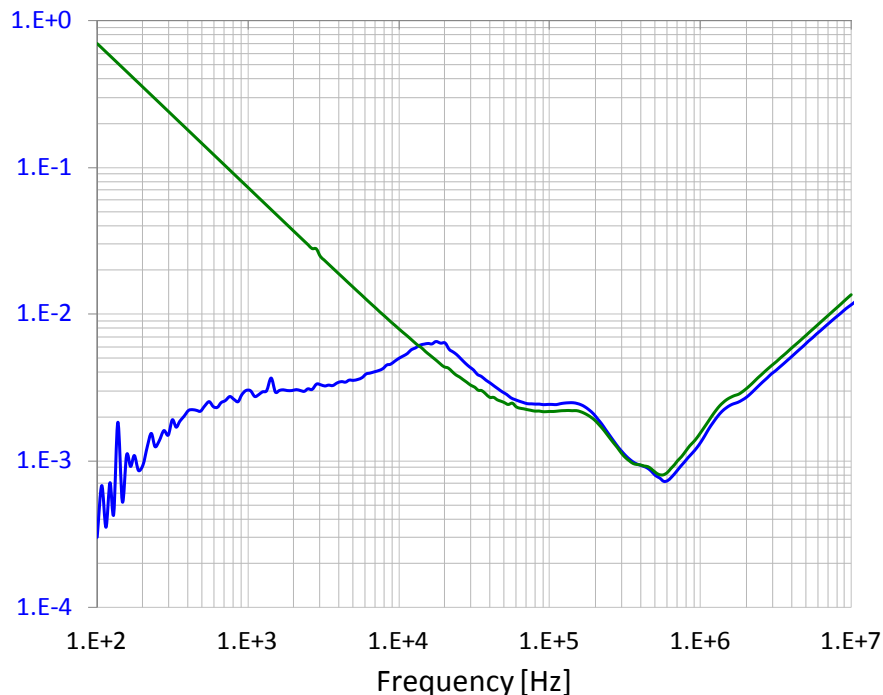


Measured gain magnitude, phase [dB, deg]

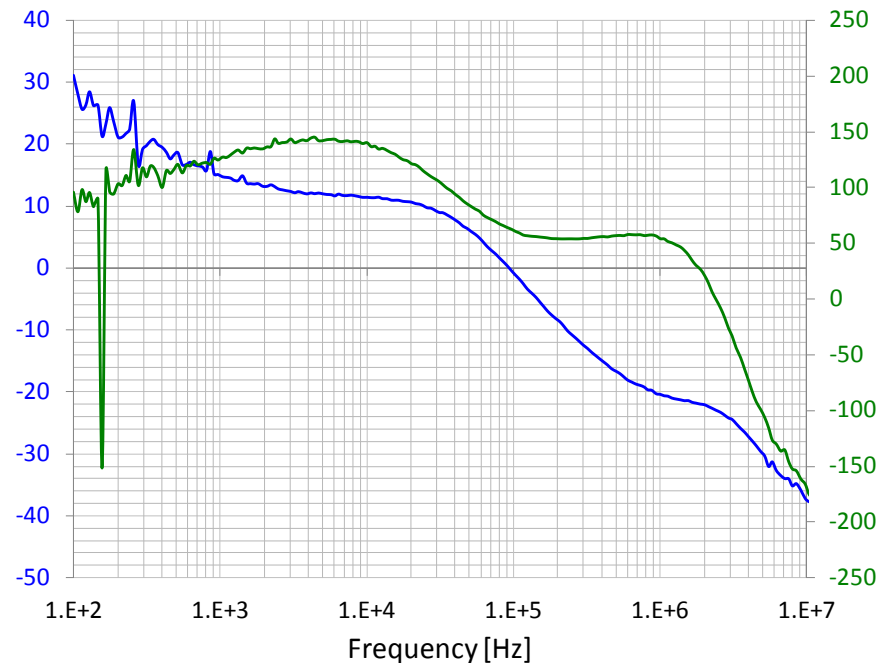


Nyquist and Stability Plots on Stable Converter

Nyquist Plot

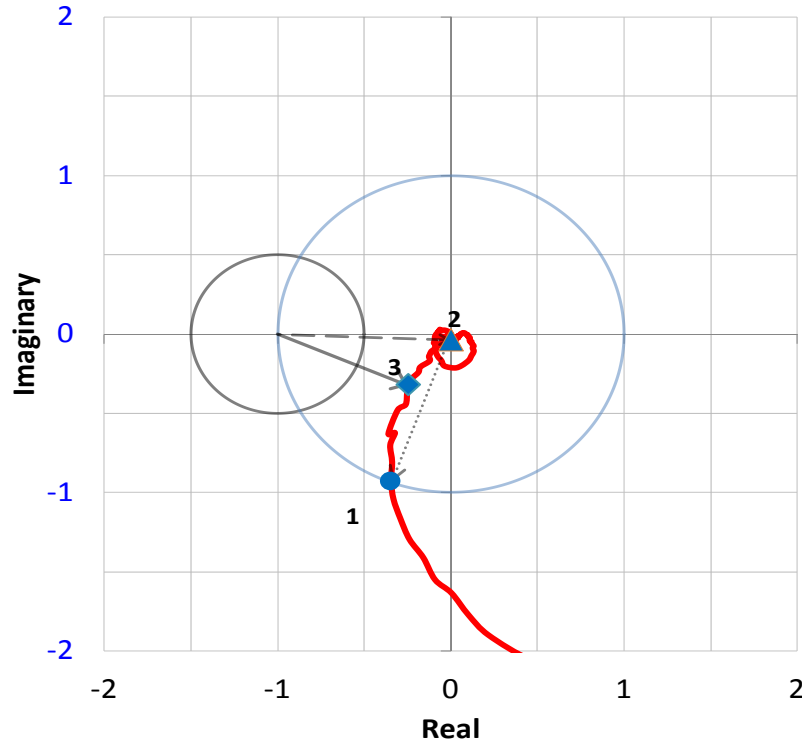

Characteristic Equation

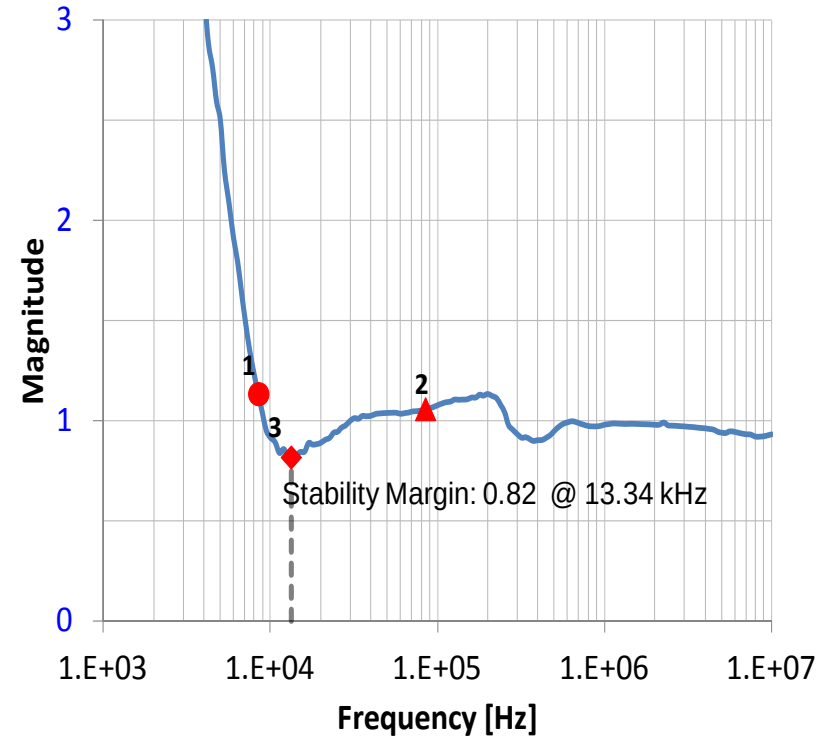

Agenda


- Introduction
- Gain-phase plots
 - Traditional gain-phase plots
 - Gain-phase plot approximations and non-invasive measurements
- Nyquist plots and Stability margin
- Other metrics
- What can go wrong?
 - Wrong test signal level
 - Spurious signals
 - Impact of test equipment and load circuit
 - Measurement location
- Summary and Conclusions



Impedance Profile and Characteristic Expression

- Impedance plot has peaks
- The lows of the Characteristic Expression occur at the same frequency points
- Direct correlation between impedance profile peaks and instability
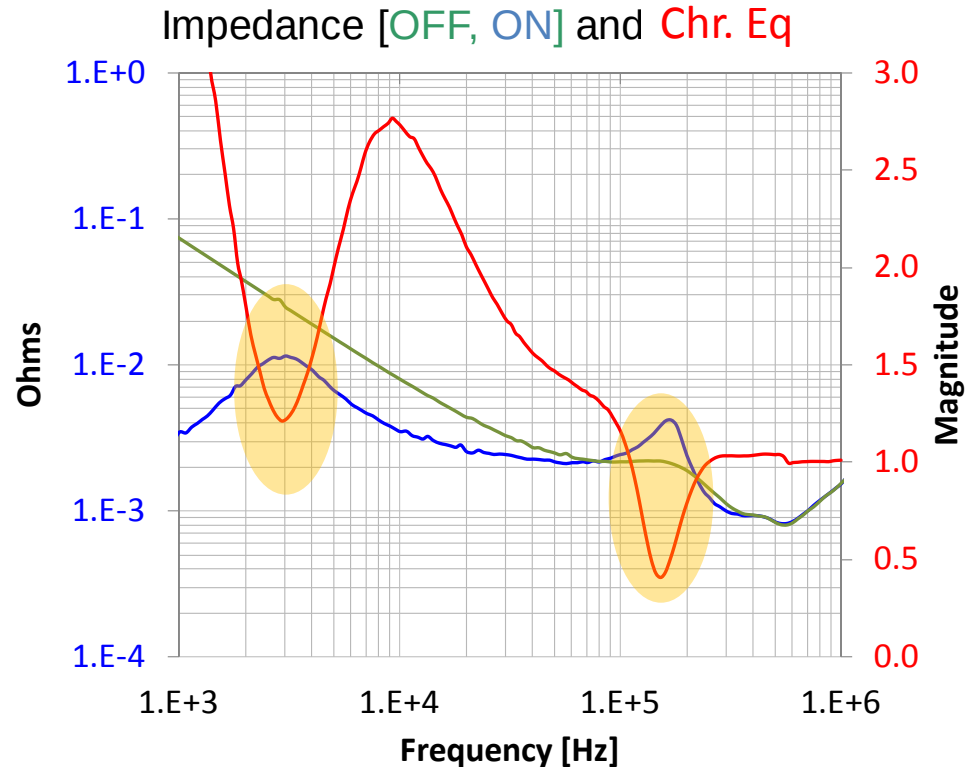
$$Z_{out-closed-loop}(f) = \frac{Z_{out-open-loop}(f)}{1 + G_{open-loop}(f)}$$







Agenda

- Introduction
- Gain-phase plots
 - Traditional gain-phase plots
 - Gain-phase plot approximations and non-invasive measurements
- Nyquist plots and Stability margin
- Other metrics
- What can go wrong?
 - Wrong test signal level
 - Spurious signals
 - Impact of test equipment and load circuit
 - Measurement location
- Summary and Conclusions



Gain-Phase Curves vs. Injection Level

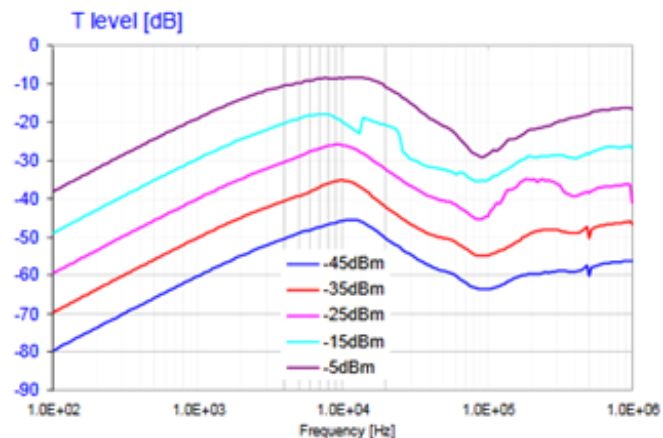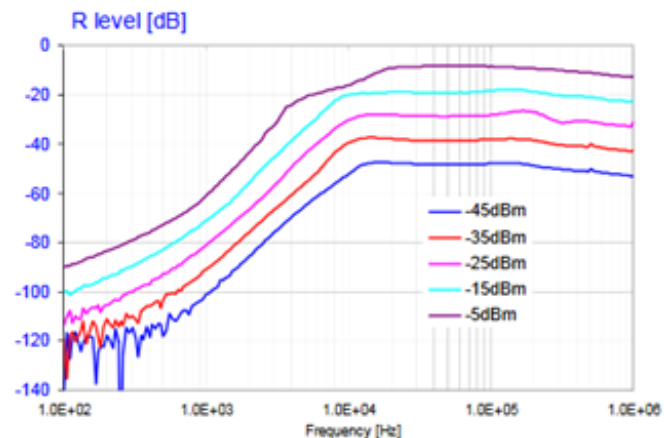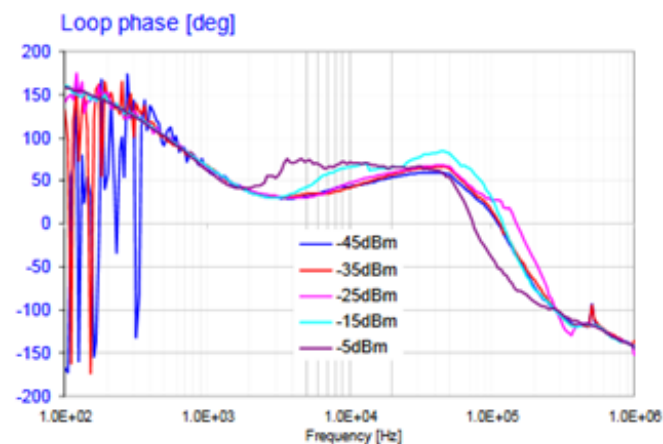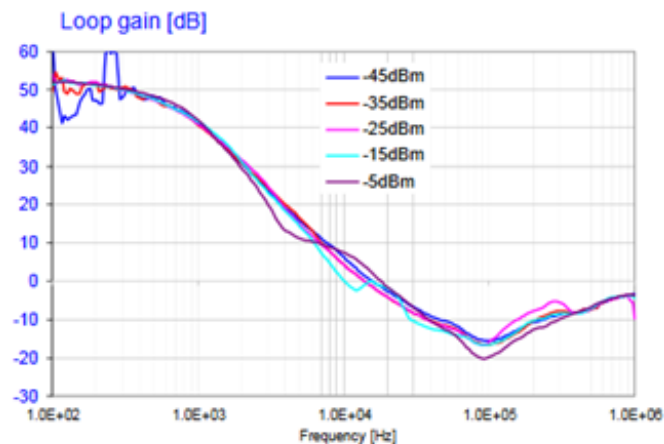- Loop gain varies several orders of magnitude over frequency
- Improper signal level can lead to saturation or noisy results







Agenda

- Introduction
- Gain-phase plots
 - Traditional gain-phase plots
 - Gain-phase plot approximations and non-invasive measurements
- Nyquist plots and Stability margin
- Other metrics
- What can go wrong?
 - Wrong test signal level
 - **Spurious signals**
 - Impact of test equipment and load circuit
 - Measurement location
- Summary and Conclusions




Impedance and Gain-Phase vs. DC Load Current

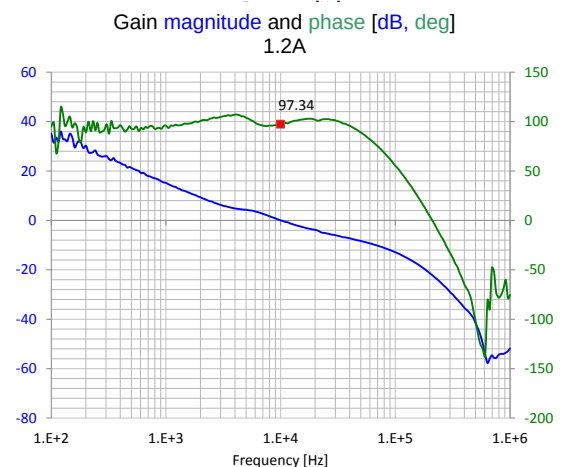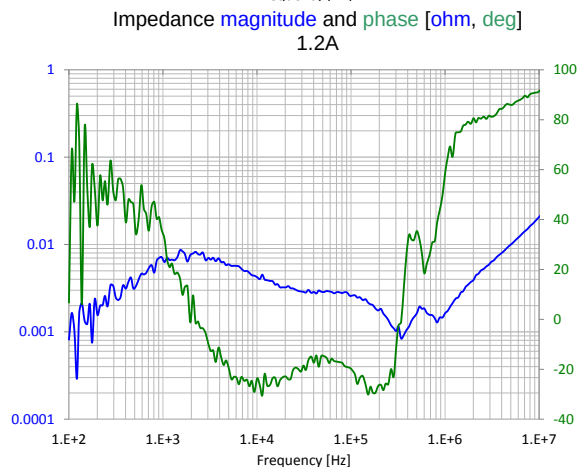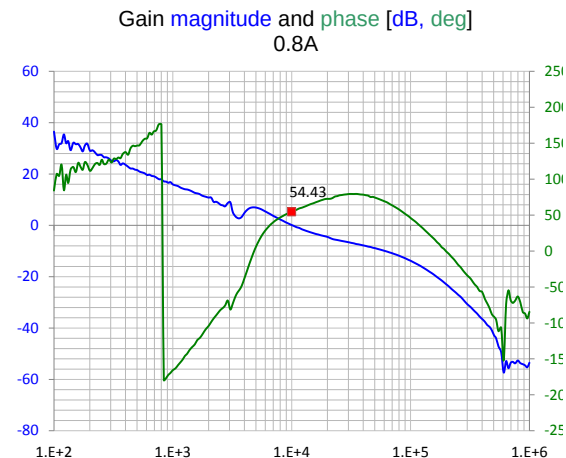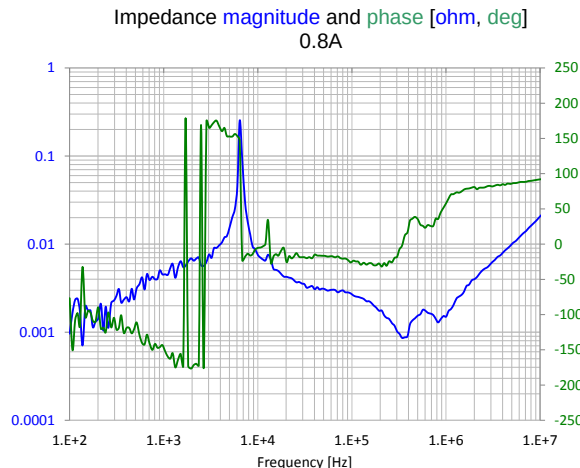- Measured small signal output impedance can be a significant function of load current
- At the same time, measured gain-phase also changes




Periodic Output Disturbance

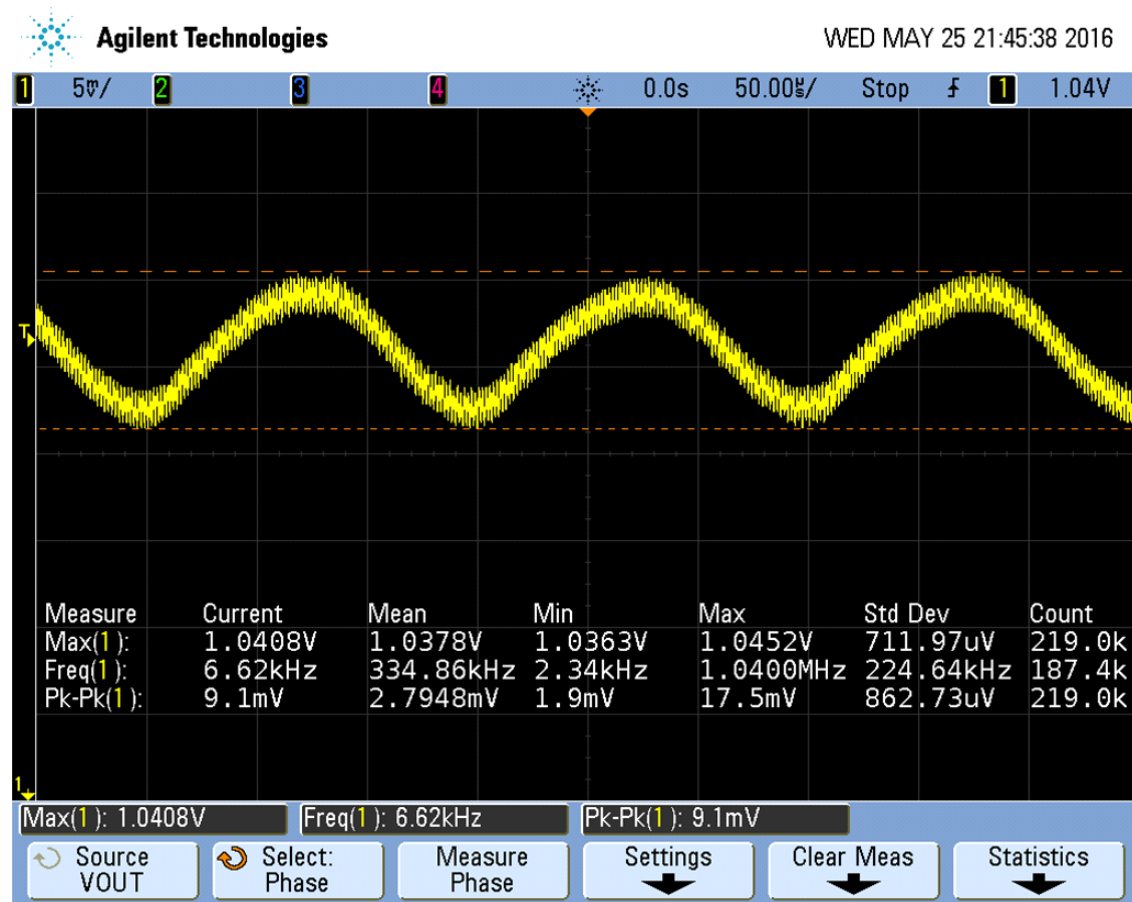- At the operating point of sudden change, a periodic, uncorrelated ripple appears



Impedance vs. Injection Level

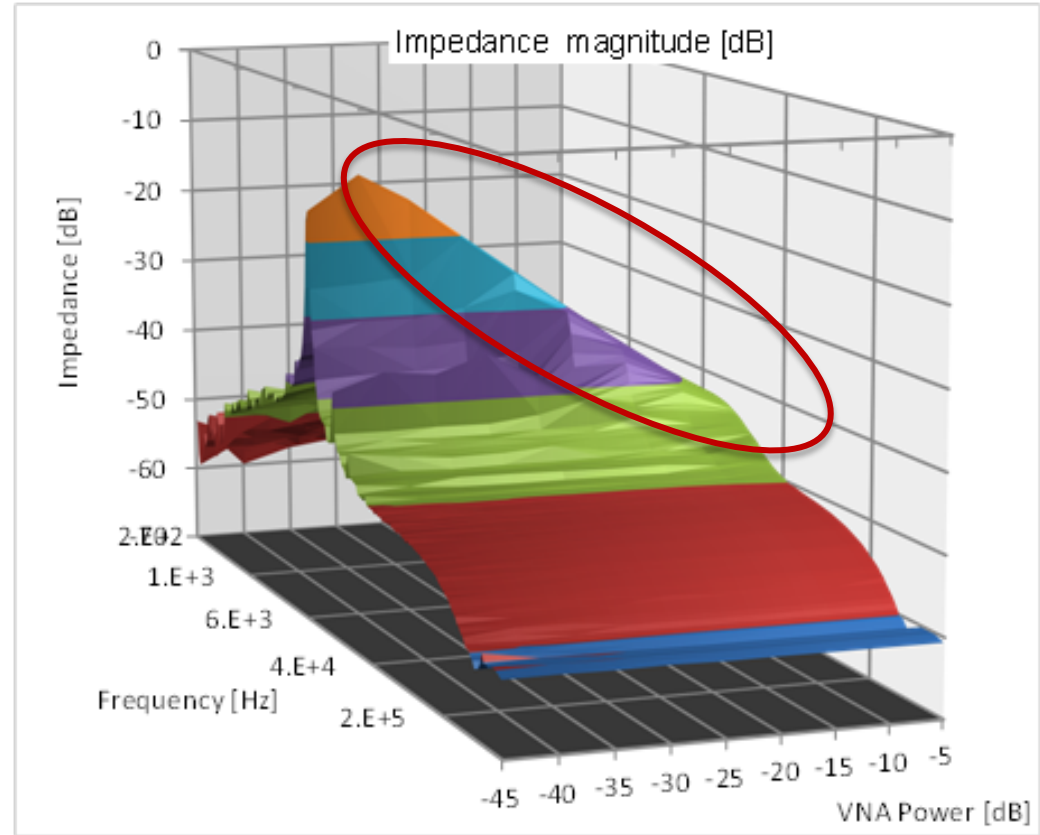- At the operating point of sudden change, the measured output impedance linearly varies with injection level





Agenda

- Introduction
- Gain-phase plots
 - Traditional gain-phase plots
 - Gain-phase plot approximations and non-invasive measurements
- Nyquist plots and Stability margin
- Other metrics
- What can go wrong?
 - Wrong test signal level
 - Spurious signals
 - Impact of test equipment and load circuit
 - Measurement location
- Summary and Conclusions







Impedance of Electronic Load

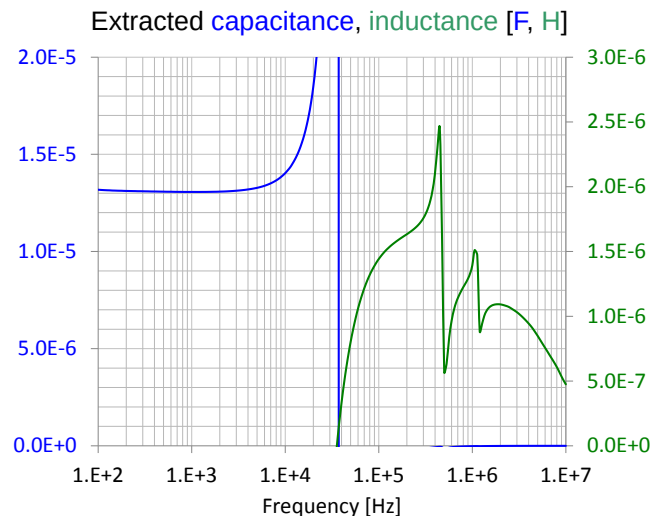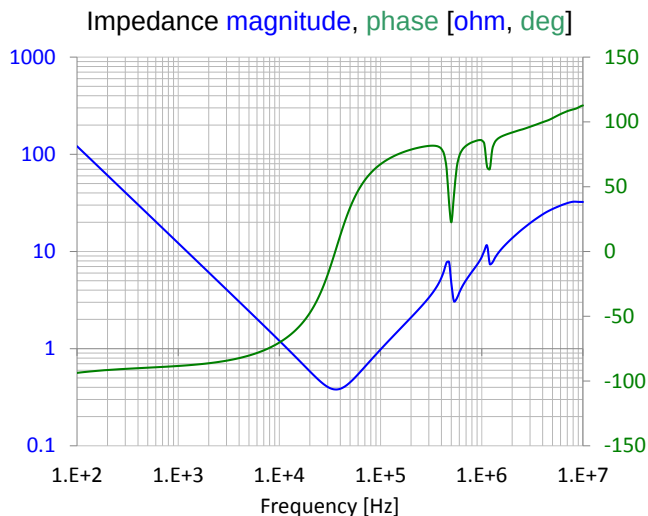- High current electronic loads have capacitors across their input
- The extra capacitance can change the DUT behavior






Effect of Electronic Load

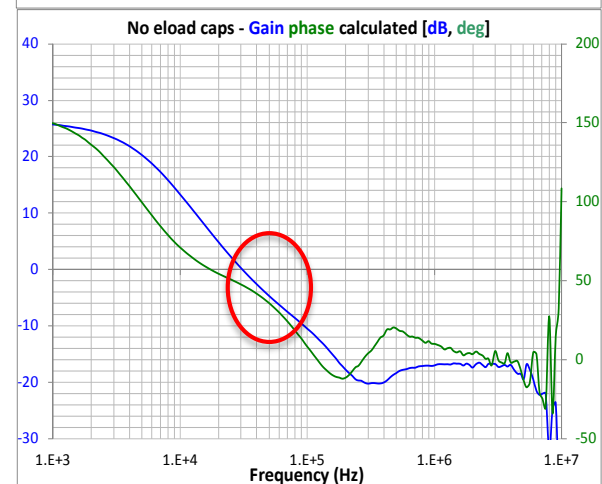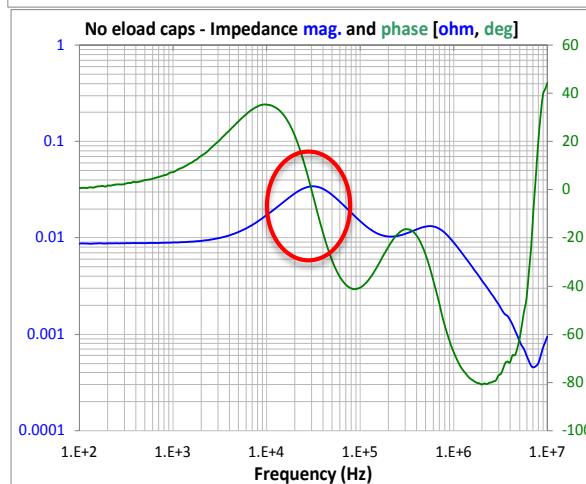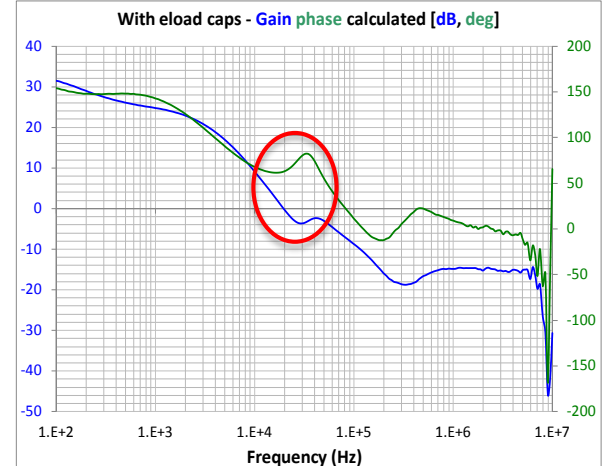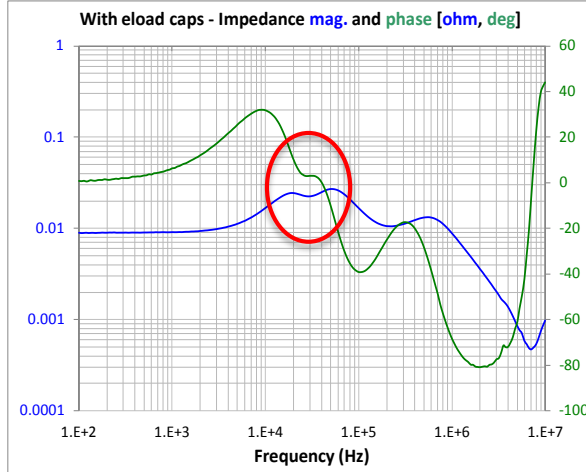- Measured output impedance and gain-phase plots with and without extra capacitance in electronic load




Impact of Secondary Output Filter

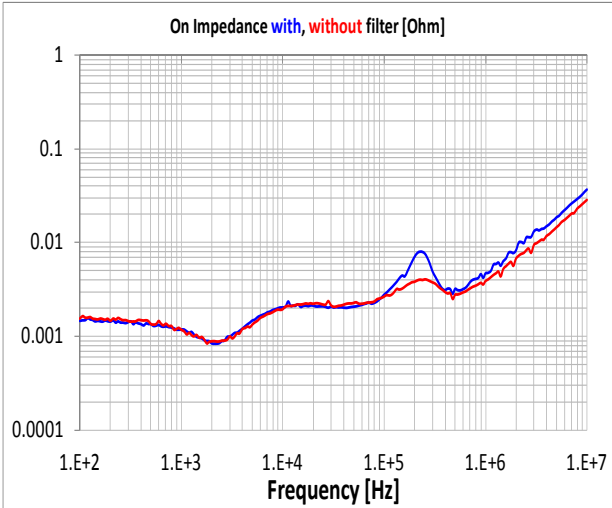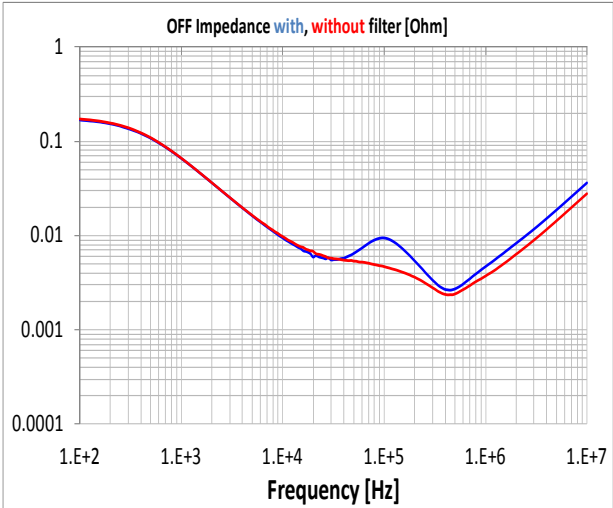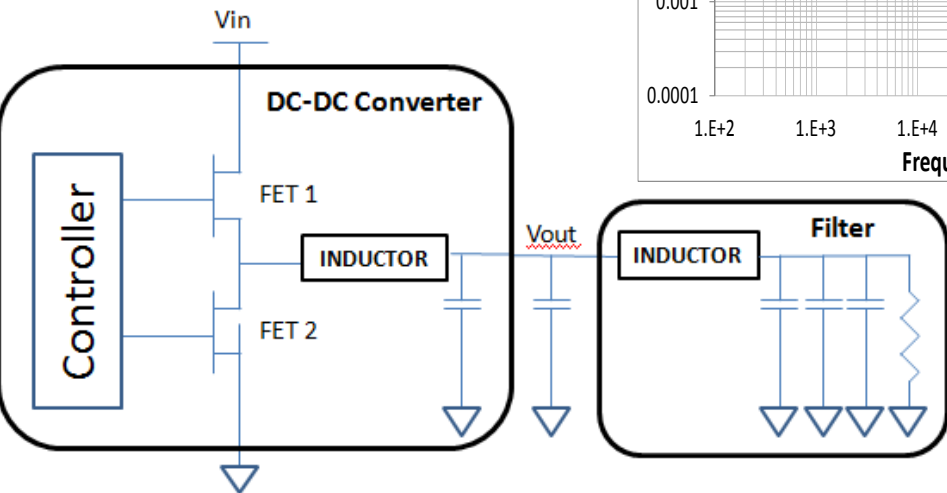

Geometry for Plane R-C Filtering

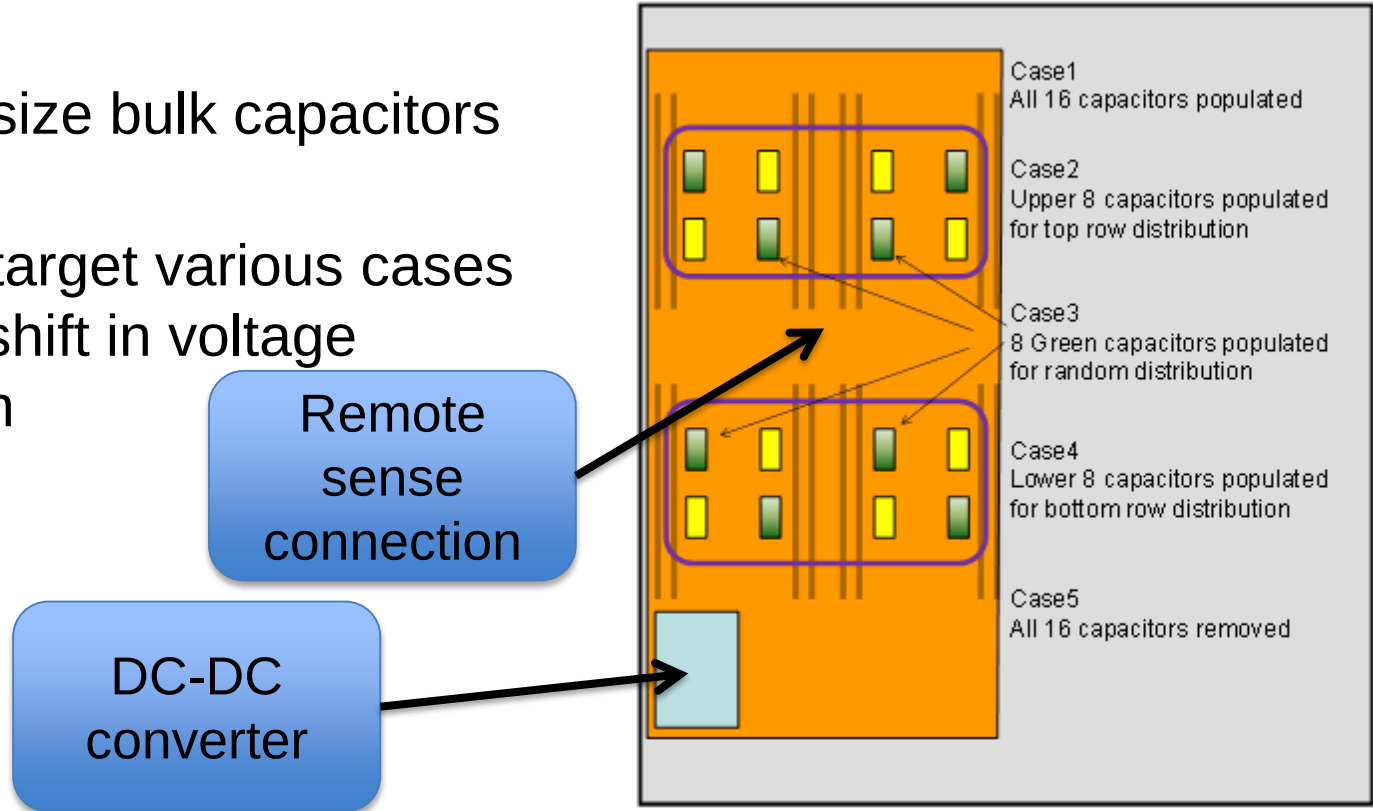- 16 - 1000uF D-size bulk capacitors populated
- Configurations target various cases of extra phase shift in voltage transfer function




"Impact of Regulator Sense-point Location on PDN Response," DesignCon 2015, Santa Clara, CA, January 27 - 30, 2015




Plane R-C Filtering

Voltage Transfer magnitude [-]

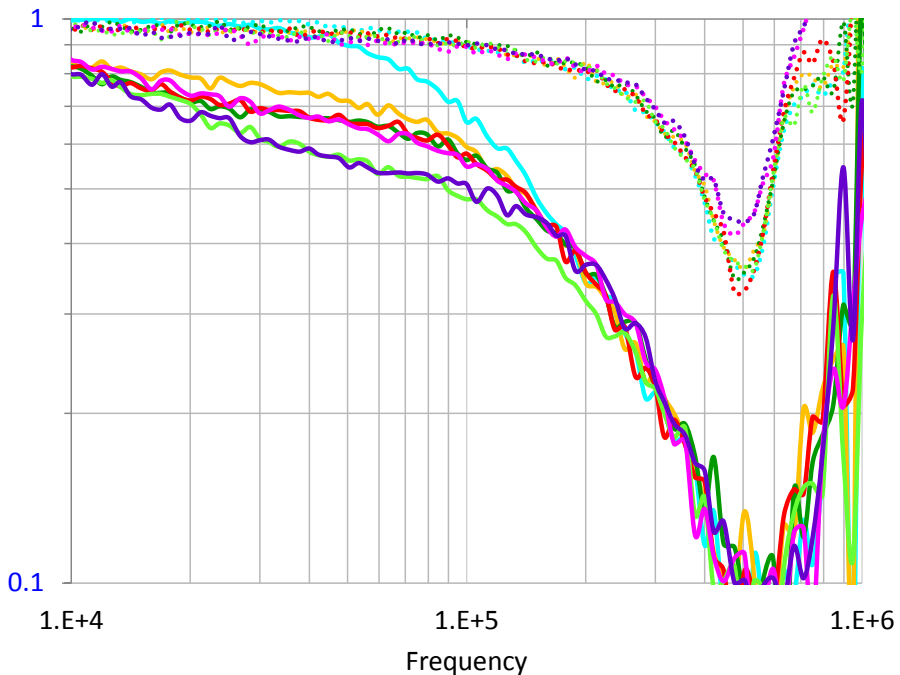

Voltage Transfer phase [deg]




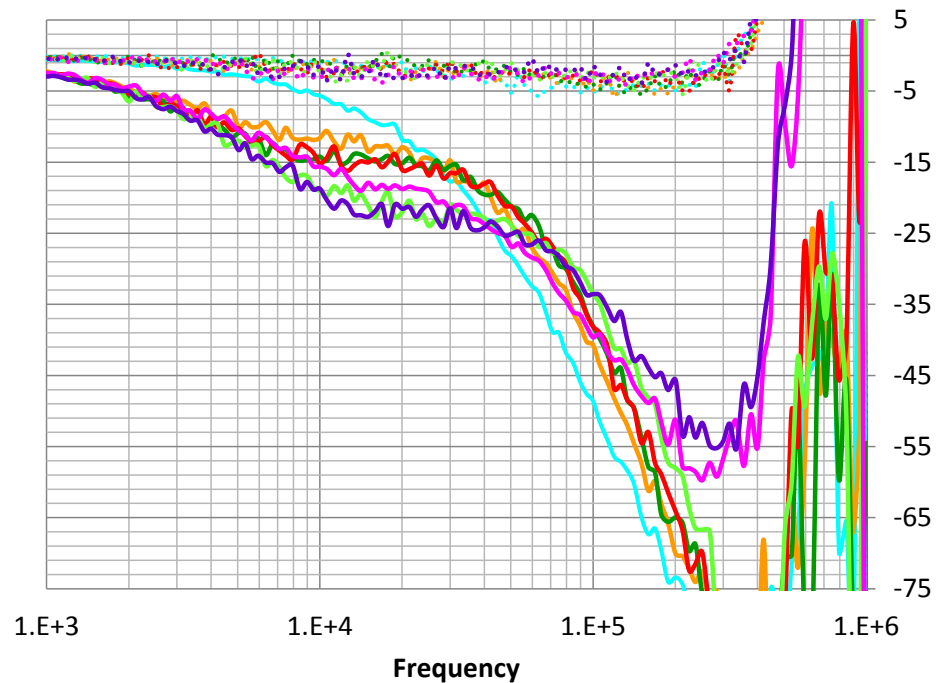


Agenda


- Introduction
- Gain-phase plots
 - Traditional gain-phase plots
 - Gain-phase plot approximations and non-invasive measurements
- Nyquist plots and Stability margin
- Other metrics
- What can go wrong?
 - Wrong test signal level
 - Spurious signals
 - Impact of test equipment and load circuit
 - **Measurement location**
- Summary and Conclusions



Effect of Measurement Location

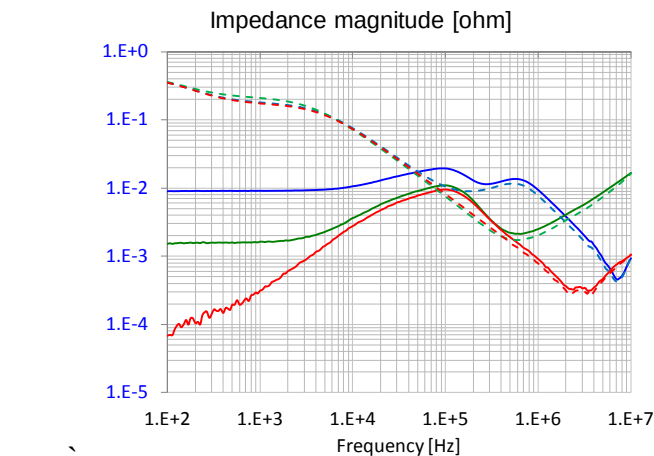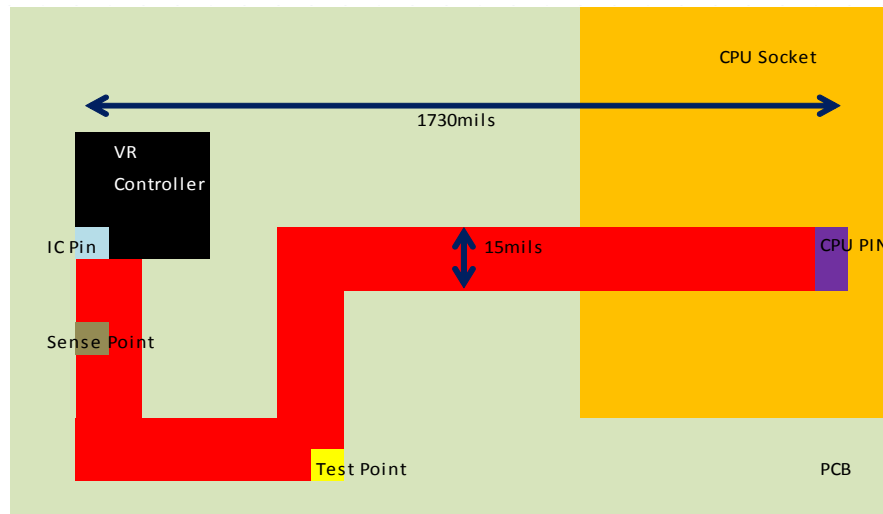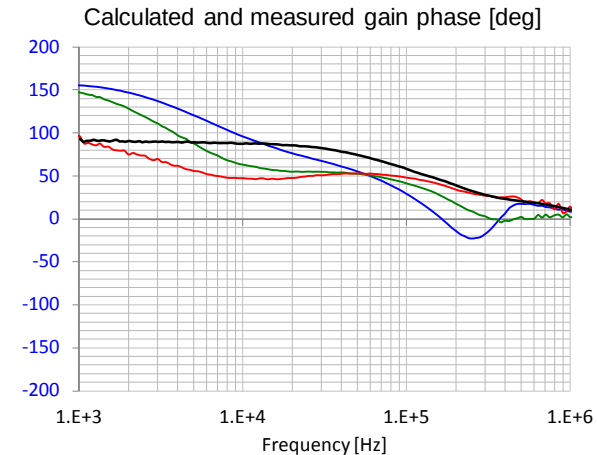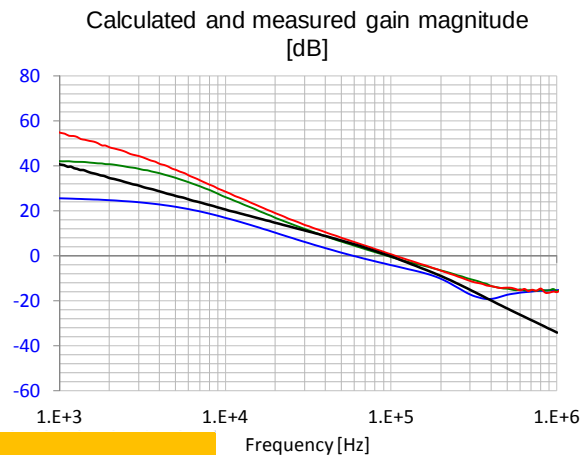

Effect of Measurement Location

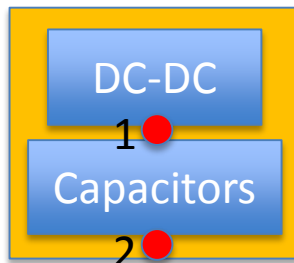

Green


Sense: 1, Measure: 2

Blue

Sense: 2, Measure: 2

Red

Sense: 2, Measure: 1

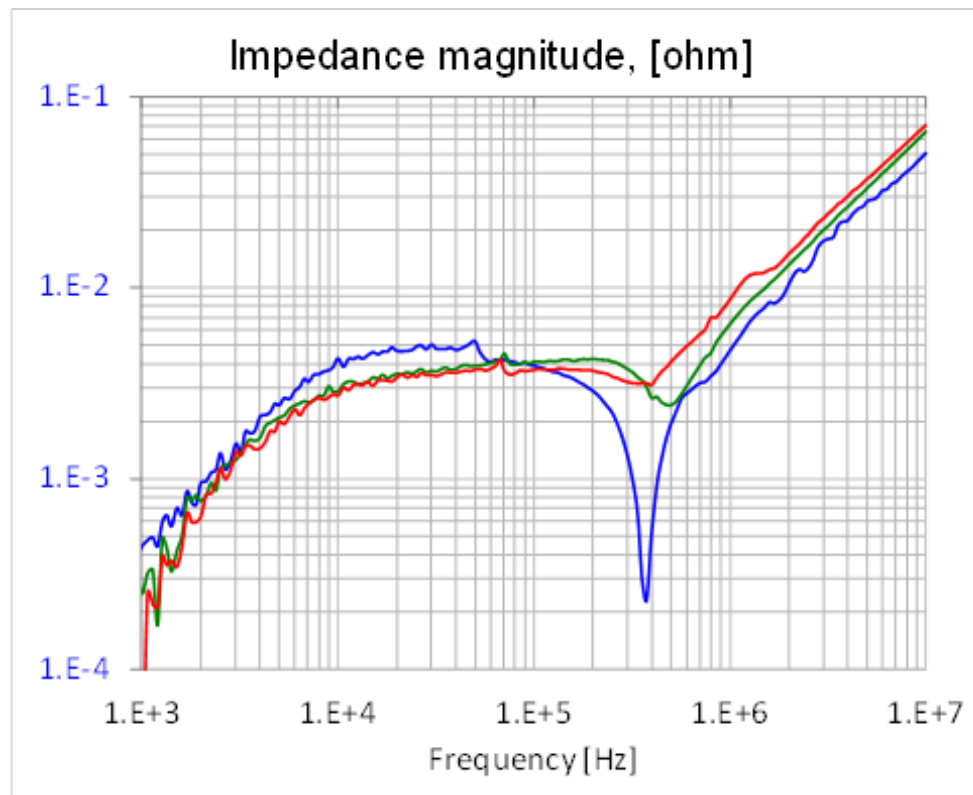

Agenda

- Introduction
- Gain-phase plots
 - Traditional gain-phase plots
 - Gain-phase plot approximations and non-invasive measurements
- Nyquist plots and Stability margin
- Other metrics
- What can go wrong?
 - Wrong test signal level
 - Spurious signals
 - Impact of test equipment and load circuit
 - Measurement location
- Summary and Conclusions



Summary and Conclusions

- Phase and gain margins are useful metrics only in special cases
- Nyquist plot, Characteristic expression and Stability margin plots provide specific views of DUT stability conditions
- Direct loop gain measurement is invasive but most robust
- NISM is noninvasive, works well with low-noise peaky impedance profiles
- Loop gain calculated from OFF and ON impedances is minimally invasive, but measurement location matters
- Measuring the loop gain function requires careful setting of injection power
- Frequency-domain measurements are invalid if uncorrelated tracking spurious signals are generated by the DUT



Thank you!

QUESTIONS?

