 


How Spatial Variation of Voltage Regulator Output Impedance Depends on Sense Point Location

Alejandro 'Alex' Miranda, (Oracle Corporation)
Joseph 'Abe' Hartman, (Oracle Corporation)
Kavitha Narayandass, (Oracle Corporation)
Ethan Koether, (Oracle Corporation)
Gustavo Blando, (Oracle Corporation)
Istvan Novak, (Oracle Corporation)



SPEAKER




Istvan Novak

Senior Principal Engineer, Oracle Corporation
istvan.novak@oracle.com

Istvan is a Senior Principle Engineer at Oracle. Besides signal integrity design of high-speed serial and parallel buses, he has been engaged in the design and characterization of power-distribution networks and packages for mid-range servers. He creates simulation models, and develops measurement techniques for power distribution. Istvan has twenty plus years of experience with high-speed digital, RF, and analog circuit and system design. He is a Fellow of IEEE for his contributions to signal-integrity and RF measurement and simulation methodologies and has twenty five patents in the areas of power distribution design and precision measurements.




Introduction

 

In competitive designs spatial attenuation and delay can not be ignored



The Noise Budget

 

Assuming LTI system and flat impedance:


$$Z_{target} = \frac{\Delta V}{\Delta I}$$

$$\Delta V = (V_{max} - V_{min}) - DC_drop - PARD$$





Non-flat Impedance: Depth of a Single Notch

Frequency domain

 


Time domain

  

SPICE deck



 Non-flat Impedance: Depth of a Single Notch



Worst-case transient noise




- Increases as depth of notch increases
- Relative increase is proportional at small blips
- Saturates at about 2x extra noise



Non-flat Impedance: Number of Notches

Worst-case transient noise

   - Increases with the number of notches
- Effect is additive for widely separated dips




Correlation, DUT1: Measurement Location

DUT


- $V_{in} = 4.5V$
- $V_{out} = 1.2V$
- 1.5A DC load current
- 0.5A_{pp} transient step

Instruments can be connected in a multitude of ways


 
- Across output terminals
(**correct**)
- Across output capacitor
(**wrong**)



Correlation: Wrong Location

 

  Low-ESR capacitors form resonant attenuators with via and pad impedance




Correlation: Correct Location



Impedance curves:

- Measured with 0dBm VNA source power
- Calculated from falling transient response
- Calculated from rising transient response

Impedance vs. frequency

 

Normalized transient response

  


Logarithmic horizontal scale

Transient curves:

- Measured falling response with oscilloscope
- Inverted rising response with oscilloscope
- Calculated from impedance



 Step Response Details for Reverse Pulse Technique




Time (μs)	Vout (V)
0	1.184
6.143	1.123
21.37	1.184
29.82	1.179
42.99	1.184
50.04	1.182

- Falling Step Response
- 1.5A DC load
- 0.5A step current
- Averaged to suppress switching ripple



 
Worst-Case Noise from Reverse Pulse Technique



- Worst-case pattern
- 0.5A current steps
- Averaged to suppress switching ripple



Nonlinear Response

 


Distorted Data: Wrong Connections



Impedance curves:

- Measured with 0dBm VNA source power
- Calculated from falling transient response
- Calculated from rising transient response

Impedance vs. frequency

 

Normalized transient response

  

Logarithmic horizontal scale

Transient curves:

- Measured falling response with oscilloscope
- Inverted rising response with oscilloscope
- Calculated from impedance




Wrong Connections, Added Capacitor

Impedance curves:

- Measured with 0dBm VNA source power
- Calculated from falling transient response
- Calculated from rising transient response

1500 μ F
polymer
tantalum
capacitor
added to the
output


Impedance vs. frequency

 


Transient curves:

- Measured falling response with oscilloscope
- Inverted rising response with oscilloscope
- Calculated from impedance


Normalized transient response

 


 
Added Capacitor, Worst-Case Transient Noise



Time (μs)	Vout (V)
0	1.183
33.63	1.171
164.4	1.185
303.7	1.183
433.0	1.182
565.0	1.1823

 


Location of Connections, DUT2

  

Output impedance curves at three different combinations of sense-point and measurement locations (from [8]). Red curve: measure at point 1, sense connected to point 2. Green curve: measure at point 2, sense connected to point 1. Blue curve: measure at point 2, sense connected to point 2.




Location of Connections, DUT2

 

- Impedance measured with VNA
- Impedance measuring cables are Cable1 and Cable2
- Three sense-point connections


DUT2, Zout, Connection Scheme A

 

Coupling in connecting cable pigtail results in unrealistically low impedance at SRF.




DUT2, Gain-phase, Connection Scheme A

 

72.51 degree phase margin




DUT2, Zout, Connection Scheme B

 

Coupling in connecting
cable pigtail is at
acceptable level.




DUT2, Gain-phase, Connection Scheme B

 

72.29 degree phase margin



DUT2, Zout, Connection Scheme C

 


Coupling in connecting
cable pigtail is at
acceptable level.



DUT2, Gain-phase, Connection Scheme C


Gain magnitude and phase [dB, deg]

 

 72.43 degree phase margin







Impedance Variation by Design Choice, DUT3



- Core rail for two ASICs
- Rectangles show core pin arrays
- DC-DC converter in the middle
- Sense-point options:
 - At ASIC1
 - At ASIC2
 - Average of ASIC1 and ASIC2
 - At DC-DC converter output




DUT3, Measurement Locations

    

- Two-port connections in the ASIC core pinfield
- Option1: self impedance across adjacent pad pairs (top)
- Option2: partial transfer impedance (top)
- Option3: transfer impedance pad-to-capacitor (bottom)

DUT3, Option1

 

- Self impedance at ASIC1 pinfield


Sense connection:

- Case1: at ASIC1
- Case2: at ASIC2
- Case3: ASIC1 and ASIC2 average
- Case4: DC-DC output

Cases differ only below the crossover frequency



DUT3, Option2

 

Partial transfer impedance
at ASIC1 pinfield

Sense connection:


- Case1: at ASIC1
- Case2: at ASIC2
- Case3: ASIC1 and ASIC2 average
- Case4: DC-DC output

Cases differ only below the
crossover frequency

Deeper notch



DUT3, Option3

 

Pad-to-capacitor transfer impedance at ASIC1 pinfield

Sense connection:

- Case1: at ASIC1
- Case2: at ASIC2
- Case3: ASIC1 and ASIC2 average
- Case4: DC-DC output

Cases differ below the crossover frequency and at SRF



Conclusions

- For linear and time invariant systems, time and frequency domain results are equivalent
- Connections must be identical
- Worst-case transient noise increases with depth of notch in impedance
- Noise increase is additive for multiple notches
- Measurement probe placed on capacitor will alter data
- Further away from sense points the impedance is also influenced by plane resistance



Thank you!

QUESTIONS?

